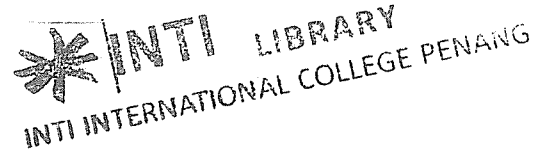


**INTI**

INTERNATIONAL COLLEGE PENANG (507232-U)  
LAUREATE INTERNATIONAL UNIVERSITIES

FINAL  
Examination Paper  
(COVER PAGE)



Session : August 2012

Programme : DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING (DEEI)

Course : EEE1102 : ELECTRONIC DEVICES AND CIRCUIT THEORY I

Date of Examination : 11 December 2012

Time : 11a.m. – 1p.m. Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

Materials permitted :

Non Programmable Scientific Calculator


Materials provided :

Nil

Examiner(s) : Liong Han Wen

Moderator :

*This paper consists of 7 printed pages, including the cover page.*

 INTI LIBRARY  
INTI INTERNATIONAL COLLEGE PENANG

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME  
(DEEI)

EEE 1102 : ELECTRONIC DEVICES AND CIRCUIT THEORY 1  
FINAL EXAMINATION : AUGUST 2012 SESSION

**Instructions:** This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks. The marks allocated to each sub-question are shown in brackets at the right-hand margin.

**Question 1**

- a. Find the average value of the full wave rectified voltage waveform as shown in Figure Q1(a). (5 marks)


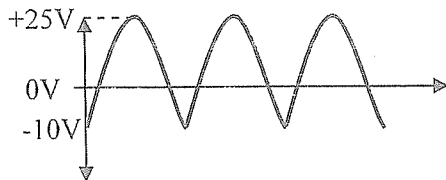


Figure Q1(a)

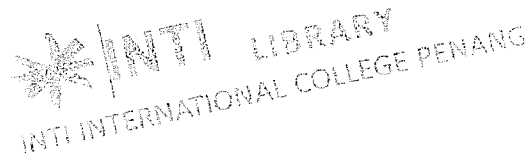

- b. Explain what is intrinsic semiconductor. (2 marks)
- c. Explain what is Peak Inverse Voltage (PIV) of a diode. (2 marks)
- d. Determine the  $V_{OUT}$  for the circuit shown in Figure Q1(d). Assume all diodes are ideal. (4 marks)

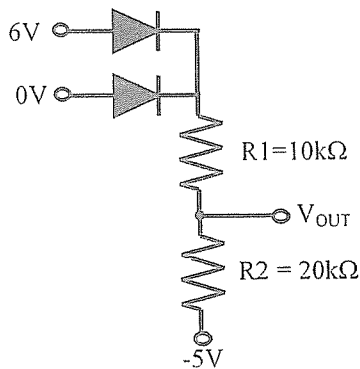


Figure Q1(d)

- e. Sketch the block diagram for the internal function block of a basic DC voltage power supply with AC input voltage. Describe the function of each module. (12 marks)

Question 2

a. Sketch the output waveform( $V_{OUT}$ ) of the following rectifier circuits. The input waveform is shown in Figure Q2(a). Assume all the diodes in this part are ideal.


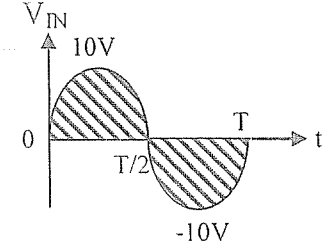


Figure Q2(a)

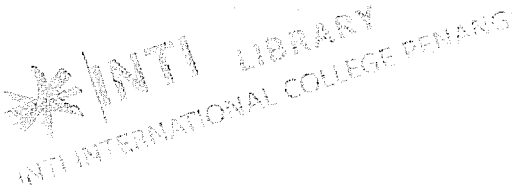

- b. For circuit shown in Figure Q2(b), to what value must R be adjusted in Figure below to make  $I_Z = 50\text{mA}$  ? Assume  $V_Z = 10\text{V}$  at  $30\text{mA}$  and  $Z_Z = 40\Omega$ . (6 marks)

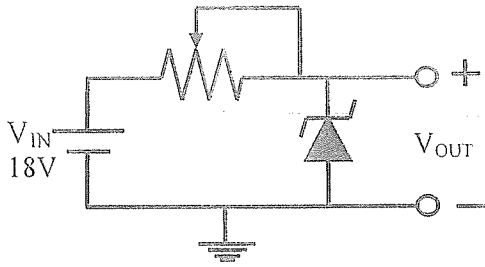


Figure Q2(b)

ANTI LIBRARY  
INTERNATIONAL COLLEGE DENMARK

Question 3

- a. Sketch a DC load line and AC load line for the circuit shown in Figure Q3(a) with a common graph. Assume  $\beta_{DC}$  and  $\beta_{ac}$  is equal to 100. (15 marks)

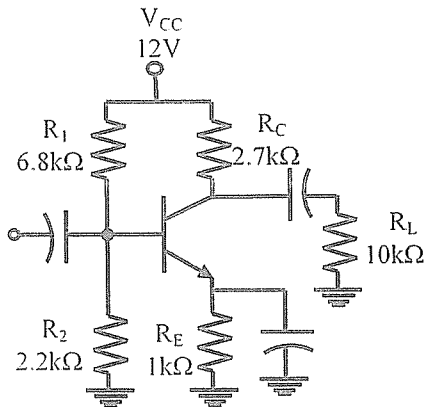


Figure Q3(a)

- b. An npn transistor is to be operated at a collector current of  $50\text{mA}$ . How high can  $V_{CE}$  be without exceeding a maximum power of  $1.2\text{W}$ ? (3 marks)
- c. Determine the  $I_{C(sat)}$  for the transistor in Figure Q3(c). What is the necessary value of  $I_B$  to produce saturation? What minimum value of  $V_{IN}$  is necessary for saturation? Assume  $V_{CE(sat)} = 0\text{V}$ . (7 marks)

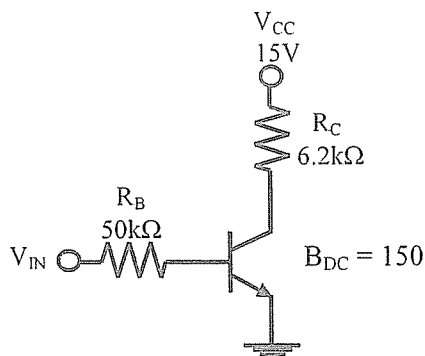


Figure Q3(c)

Question 4

- a. The base bias circuit in Figure Q4(a) is subjected to a temperature variation from 0°C to 70°C. The  $\beta_{DC}$  decrease by 50 percent at 0°C and increase by 75 percent at 70°C from its nominal value of 110 at 25°C. What are the % of changes in  $I_C$  over the temperature change from 0°C to 70°C ? (7 marks)

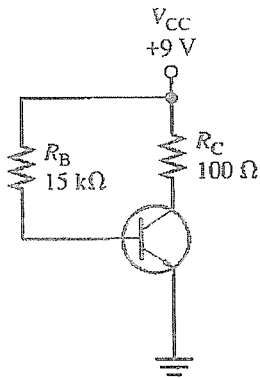


Figure Q4(a)

UNIVERSITY OF  
SOUTH ALABAMA  
INTERNATIONAL COLLEGE

- b. For the circuit shown in Figure Q4(b), find the value of  $R_B$  that will cause the transistor just in saturation. (9 marks)

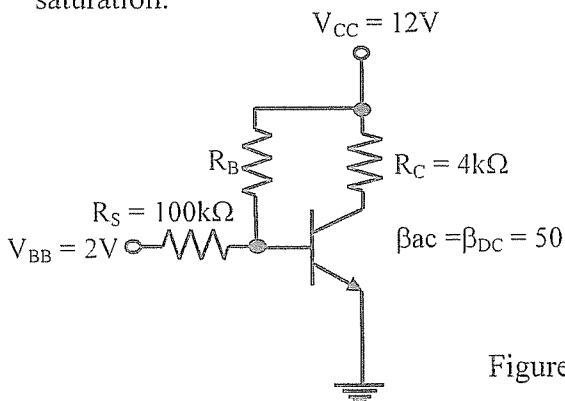


Figure Q4(b)

- c. Determine the values of  $V_C$  and  $V_B$  for the network shown in Figure Q4(c). Assume  $\beta_{DC} = 100$ . (9 marks)


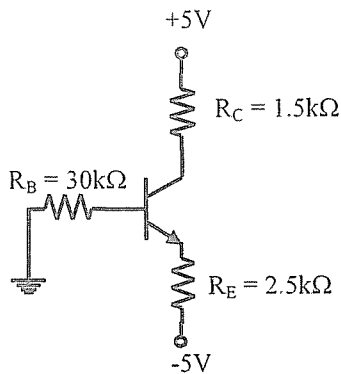


Figure Q4(c)


**Question 5**

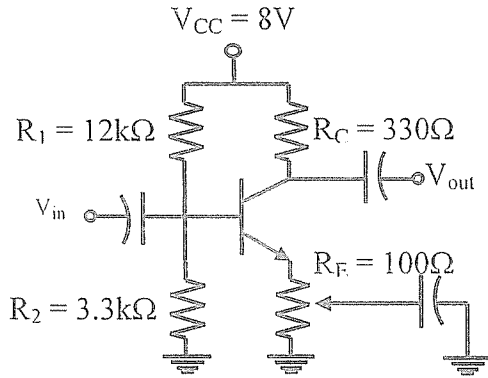- a. The amplifier in Figure Q5 (a) has a variable gain control, using  $100\Omega$  potentiometer for  $R_E$  with wiper ac grounded. As the potentiometer is adjusted, more or less of  $R_E$  is bypassed to ground, thus varying the gain. The total  $R_E$  remains constant to dc, keeping the bias fixed. Determine the maximum and minimum gains for this unloaded amplifier. (14 marks)



$\beta_{DC} = 150$   
 $\beta_{ac} = 150$

Figure Q5(a)

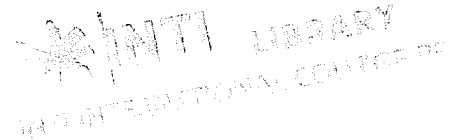

- b. For the transistor circuit shown in Figure Q5b, determine the DC value of :

- i.  $I_E$  (4 marks)
- ii.  $V_C$  (3 marks)
- iii.  $V_{CE}$  (4 marks)

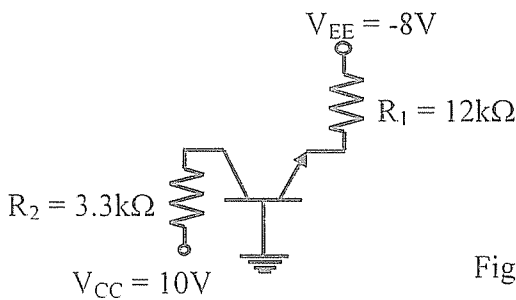


Figure Q5b

**Question 6**

- a. Sketch the construction of Depletion MOSFET(both p and n channel). What is the difference in the operation of D-MOSFET and E-MOSFET? (6 marks)
- b. Given a D-MOSFET with  $I_{DSS} = 10\text{mA}$  and  $V_{GS(off)} = -8\text{V}$ .
- (i) What type of the D-MOSFET is? Why? (2 marks)
  - (ii) Calculate  $I_D$  at  $V_{GS} = -3\text{V}$  (2 marks)
  - (iii) Calculate  $I_D$  at  $V_{GS} = +3\text{V}$  (2 marks)

