

INTI

International College Penang

LAUREATE INTERNATIONAL UNIVERSITIES®

INTI INTERNATIONAL COLLEGE PENANG
LIBRARY

FINAL
Examination Paper

(COVER PAGE)

Session : AUGUST 2012

Programme : Diploma in Electrical and Electronic Engineering (DEEI)

Course : EEE2101 : INTRODUCTION TO DIGITAL ELECTRONICS

Date of Examination : _____

Time : _____ Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet Provided. All questions carry equal marks.

Students are not allowed to remove this question paper from the examination venue.

Materials permitted : Non-programmable scientific calculator

Materials provided : Appendix-1 and Appendix-2

Examiner(s) : Chan Tse Wei

Moderator : _____

INTI LIBRARY
INTI INTERNATIONAL COLLEGE PENANG

This paper consists of 7 printed pages, including the cover page.

Question 2

- a. A 2-input logic gate is applied with signals A and B simultaneously. The timing diagram of the input signals are shown in Figure-Q2(a) respectively.

 


Figure-Q2(a)

Draw the timing diagram (in Appendix-1) of the output signal for each of the following logic gate implementation.

- i. AND gate [4]
- ii. NOR gate [4]
- iii. XOR gate [4]

Note: Attached Appendix-1 to your answer booklet.

 


Figure-Q2(b)

- b.
 - i. Express the Boolean function of output F in sum-of-product form. [3]
 - ii. Express the Boolean function of output F in product-of-sum form. [4]
 - iii. Redraw the circuit using NAND gates only so that an active low output is implemented. [3]

- c. Show that $AB + \bar{A}C + BC = AB + \bar{A}C$ [3]

Question 4

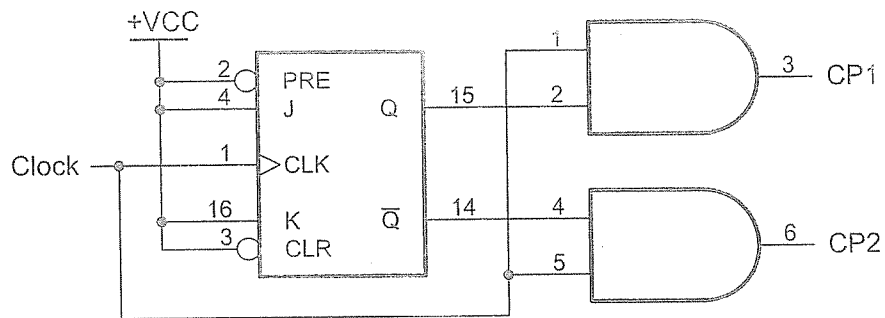


Figure-Q4(a)

- a. i. State the mode of operation of the JK flip-flop in Figure-Q4(a). [2]
- ii. Draw the timing diagram for CP1 and CP2 respectively in response to a clock signal shown in Appendix-2. [6]
- Note: Attach Appendix-2 to your answer booklet. [6]
- iii. State the application of the circuit in Figure-Q4(a). [2]
- b. A MOD-5 synchronous up counter is needed for a digital system.
- i. Draw a state diagram for the required counter; all unused states which occur will reset the counter on the next clock pulse to zero state. [2]
- ii. Produce a transition table for the counter. [4]
- iii. If JK flip-flops are to be used in the design of the counter, derive the simplest excitation expression for each flip-flop input. [9]

Question 6

- a. An 8-bit DAC produces an output current in proportion to its digital input. For a digital input of 00010100, an output current of 10mA is produced.
- What will the output current be if the digital input is 00011101? [3]
 - What is the maximum output current produced by this DAC? [3]
 - What should the digital input be if a 100mA output current is required? [3]
- b. Assume that the 8-bit DAC described in part 6(a) uses a $-5V$ to represent a digital input 1 while a $0V$ to represent digital input 0, and the load resistance is 130Ω .
- Draw an $R/2^nR$ DAC that will implement the DAC described to supply current to the 130Ω load resistor. [3]
 - Suggest all the resistances required in the DAC. [8]
 - State the main shortcoming of this type of DAC. [2]
- c. Suggest an alternative DAC that will resolve the shortcoming of the DAC stated in part 6(b)(iii). Draw the schematic diagram of the suggested DAC. [3]

 INTI LIBRARY
INTI INTERNATIONAL COLLEGE PENANG


– THE END –

Appendix 1

Student Name:	
Student ID:	

Question 2

a.

 

i. AND gate:

.....

.....

ii. NOR gate:

.....

.....

iii. XOR gate:

.....

.....

Appendix 2

Student Name:	
Student ID:	

Question 4(a)(ii)

