



INTI

INTERNATIONAL COLLEGE PENANG (507232-U)
LAUREATE INTERNATIONAL UNIVERSITIES

FINAL
Examination Paper

(COVER PAGE)

Session : APRIL 2013

Programme : DIPLOMA IN ELECTRICAL AND ELECTRONIC
ENGINEERING

Course : EEE 2101: INTRODUCTION TO DIGITAL ELECTRONICS

Date of Examination : 29 July 2013

Time : 5p.m. – 7p.m. Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Materials permitted :

Non-Programmable Scientific Calculator

Materials provided :

Examiner(s) : **Khoo Boo Tap**

Moderator : **Shalyn Lim Sheue Hui**

This paper consists of 7 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEE/I)

**EEE2101: INTRODUCTION TO DIGITAL ELECTRONICS
FINAL EXAMINATION: APR2013 SESSION**

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Question 1

- (a) List three advantages of digital data compared to analogue data. (3 marks)

- (b) Express the decimal number +38 and -38 as a 7-bit number in the sign-magnitude, 1's complement and 2's complement form for Table 1(b). (3 marks)

	+38	-38
Sign-magnitude		
1's complement		
2's complement		

Table 1(b)

- (c) Assuming the following binary numbers are in 2's complement system.
- i. 01100110
 - ii. 01110001
- Does the sum of the two binary numbers cause an overflow? Explain your answer. (5 marks)
- (d) Perform the following number system transformation. Show all workings clearly.
- i) $1001001.10000111011_{\text{BCD}}$ to decimal (2 marks)
 - ii) 41.6875_{10} to binary (2 marks)
 - iii) CAFE.BABE_{16} to octal (2 marks)
- (e) A 24-bit computer utilises the 2's complement signed number scheme.
- i) Determine the range of numerical value its 24-bit register holds. (4 marks)
 - ii) Describe how the computer performs the subtraction of $28_{10} - 7_{10}$ using 2's complement arithmetic. (4 marks)

Question 2

(a) Name the three basic logic gates, with their logic symbol and corresponding truth tables. (5 marks)

(b) Use Boolean algebra to:

- i) Express in standard SOP form, $P = ABC\bar{C} + \bar{C}D + ABD$
- ii) Express in standard POS form, $Q = (A + \bar{B})(\bar{B} + C)(A + \bar{C})$
- iii) Simplify, $R = \bar{A}\bar{B}C + ABC + \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C$
- iv) Simplify, $S = ABC\bar{C} + A(\bar{B} + \bar{C})(B + C)$

(12 marks)

(c) A chemical plant needs a microprocessor driven alarm system to warn of critical conditions in one of its chemical tanks. The tank has four HIGH/LOW (I/O) switches that monitor temperature (T), pressure (P), fluid level (L) and weight (W). Design a system that will notify the microprocessor to activate an alarm when any of the following conditions arise:

- High fluid level with high temperature and high pressure
- Low fluid level with high temperature and high weight
- Low fluid level with low temperature and high pressure
- Low fluid level with low weight and high temperature

(8 marks)

Question 3

(a) A full adder is a device that performs binary addition of two single input bits and a carry input bits. It output a sum (S) and a carry output (C_{out}) bit as shown in figure Q3(a) below:

 


Figure 3(a)

Generate the truth table and hence derive the simplest logic expression of S and C_{out} .

(7 marks)

(b) Using A, B, C_{in} as input and S and C_{out} as output, draw a full adder circuit using two half adders and an OR gate.

(5 marks)

(c) Consider the following combinational logic circuit in Figure 3(c):

 


Figure 3(c)

- i) Write the Boolean expression for F. (3 marks)

- ii) Assuming the complements of the variables are available, implement the function, F (in its simplest form) using
 - a) AND-OR logic
 - b) AND-OR-INVERT logic
 - c) NAND gates only
 - d) NOR gates only
 - e) 8-to-1 multiplexer(10 marks)

Question 4

- (a) For the state diagram shown in Figure 4(a) below, draw the transition table and determine the positive edge-triggered J-K flip-flop control equations before drawing the logic diagram.

 


Figure 4(a)

(14 marks)

- (b) For the pulse shown in Figure Q4(b) below, graphically determine the following:

 


Figure Q4(b)

- i) Rise time
- ii) Fall time
- iii) Pulse time
- iv) Amplitude

(4 marks)

- (c) Design a circuit comparator that gives a HIGH output if the binary input A_1A_0 is greater than B_1B_0 .
(7 marks)

Question 5

- (a) i) State the main difference between synchronous and asynchronous counters.
 ii) Discuss the advantage and disadvantage of serial transfer over parallel transfer in registers.
(4 marks)

- (b) A shift register has eight stages. If the clock frequency is 4MHz, calculate the time needed to load 8 bits of data into the register,
 i) in serial
 ii) in parallel
(4 marks)

- (c) Show the logic diagram of a 4 bit asynchronous count-up counter which uses positive edge-triggered JK flip-flops and has a propagation delay of 8ns. Also determine the total propagation delay and the maximum frequency at which the counter can be operated.
(6 marks)

- (d) Given a waveform shown in Figure Q5(d). If the waveform is applied to a sampling circuit and it is sampled every 3ms, determine the following:

 


Figure Q5(d)

- i) Draw the output of the sampling circuit. Assume a one-to-one voltage correspondence between the input and output.
(4 marks)

- ii) If the output in part (i) is applied to a hold circuit, draw the output of the hold circuit. (4 marks)
- iii) If the output in part (ii) is quantized using 4 bits, list the resulting sequence of binary codes. (3 marks)

Question 6

- a) Determine the simplified Boolean expression for the output of the circuit in Figure Q6(a) below. Draw its truth table. (5 marks)

 


Figure Q6(a)

- b) What is the meaning of the term “integrated” in integrated circuit (IC)? Why it is important in the field of electronics? (4 marks)
- c) Use a Karnaugh map to
- convert $F = ABC + \bar{A}BCD + \bar{A}B\bar{C}D + ACD$ into its minimum POS form. (4 marks)
 - convert $F = (A + B + D)(\bar{A} + \bar{C} + \bar{D})(A + \bar{B} + C)$ into its minimum SOP form. (4 marks)
 - minimize $F = \bar{A}\bar{B} + \bar{C}D + C + \bar{B}CD$ in either SOP or POS form. (4 marks)
- d) Draw the circuit of a 4-bit Serial-In-Serial-Out (SISO) shift register using only positive edge-triggered D flip-flops. Label your circuit clearly. (4 marks)

– THE END –