



INTI
International College Penang
LAUREATE INTERNATIONAL UNIVERSITIES*

FINAL
Examination Paper

(COVER PAGE)

Session : August 2017

Programmes : Diploma in Electrical and Electronic Engineering (DEEI)

Course : EEE1106: Analogue Electronics

Date of Examination : 12 December 2017 (Tuesday)

Time : 11:00am – 1:00pm

Duration : 2 Hours Reading Time Nil

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

IMPORTANT NOTE : **THIS PAPER SHOULD NOT BE TAKEN OUT OF THE EXAMINATION HALL BY THE STUDENTS.**

Materials Permitted : Scientific Calculator (Model fx570 Series)

Materials Provided : Nil

Examiner(s) : Chan Tse Wei

Moderator : Assoc. Prof. Dr. Khoo Bee Ee

This paper consists of 8 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)
 EEE1106: ANALOGUE ELECTRONICS
 FINAL EXAMINATIONS: AUGUST 2017 SESSION

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks. The marks allocated to each sub-question are shown in square brackets at the right-hand margin. Present your answers neatly and clearly. The assessor reserves the rights to ignore your answers if they are ambiguous.

Question 1

- a. Figure-Q1(a) shows the frequency response plot of a single stage AC-coupled common source amplifier evaluated with input voltages having fixed 1 V amplitude. The amplifier output is terminated with a pure resistive load.
- Estimate the mid-band voltage gain of the amplifier in dB. [4]
 - Explain the root causes of the output voltage reduction exhibited at both ends of the frequency response plot. [4]
 - Estimate the bandwidth of the amplifier. [4]

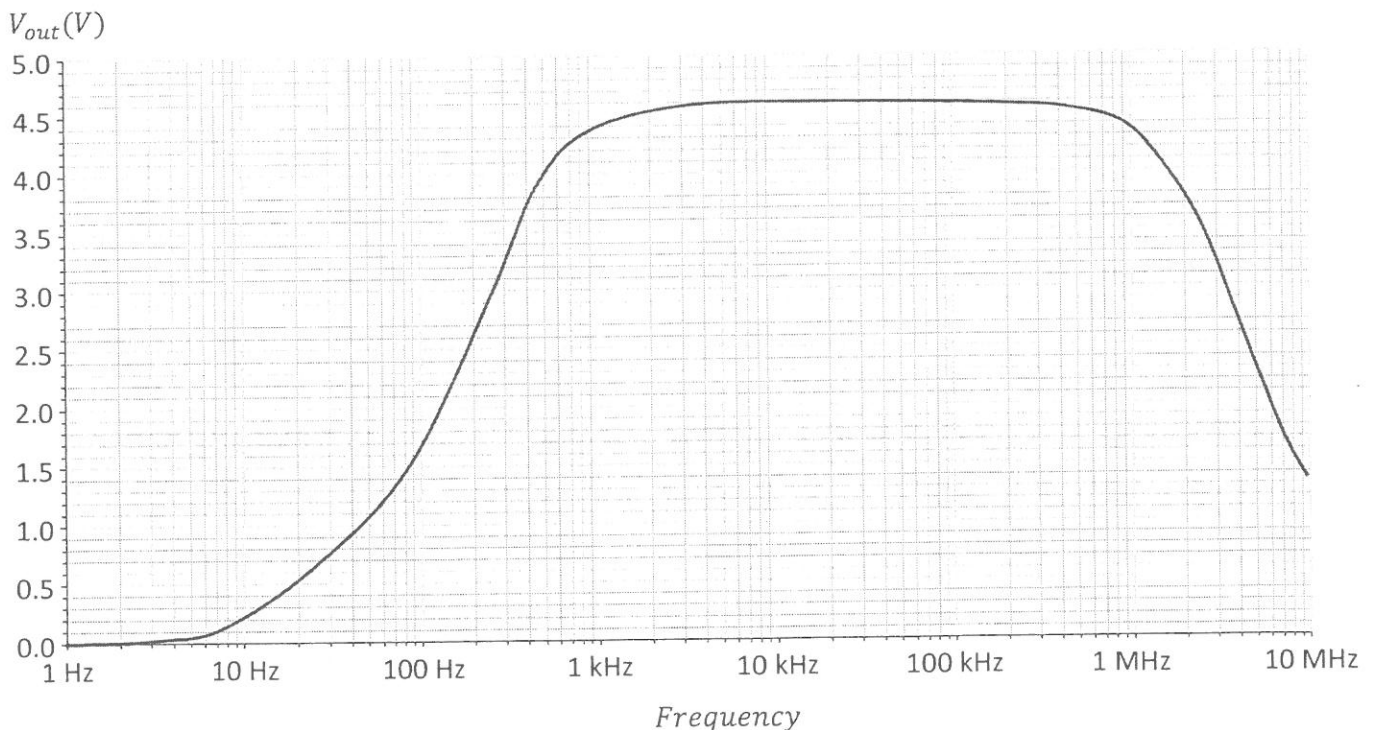


Figure-Q1(a)

- b. Figure-Q1(b) shows a JFET-based voltage amplifier. Experiment results reveal the amplifier has a maximum voltage gain, v_{out}/v_{in} of 14 dB. Use this information to estimate the transconductance (g_m) of the JFET. State any assumption made in your estimation and show all workings clearly.

[13]

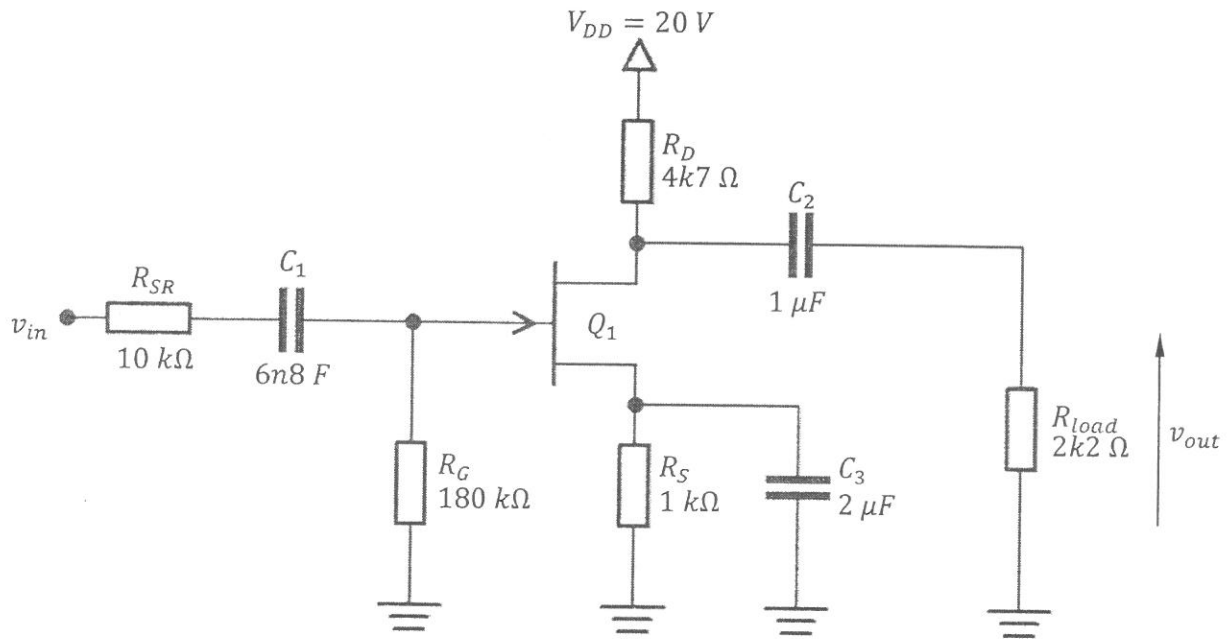


Figure-Q1(b)

Question 2

- a. Figure-Q2(a)(i) shows a power amplifier circuit. Evaluation results reveal that the amplifier has the following DC operating points:

$$V_{B_Q} = 0.48 \text{ V}$$

$$V_{C_Q} = 7.30 \text{ V}$$

Figure-Q2(a)(ii) shows the waveforms measured at port v_{in} , $V(v_{in})$ and the output voltage across resistor R_{load} , $V(V_{CC}, V_C)$.

 


Figure-Q2(a)(i)

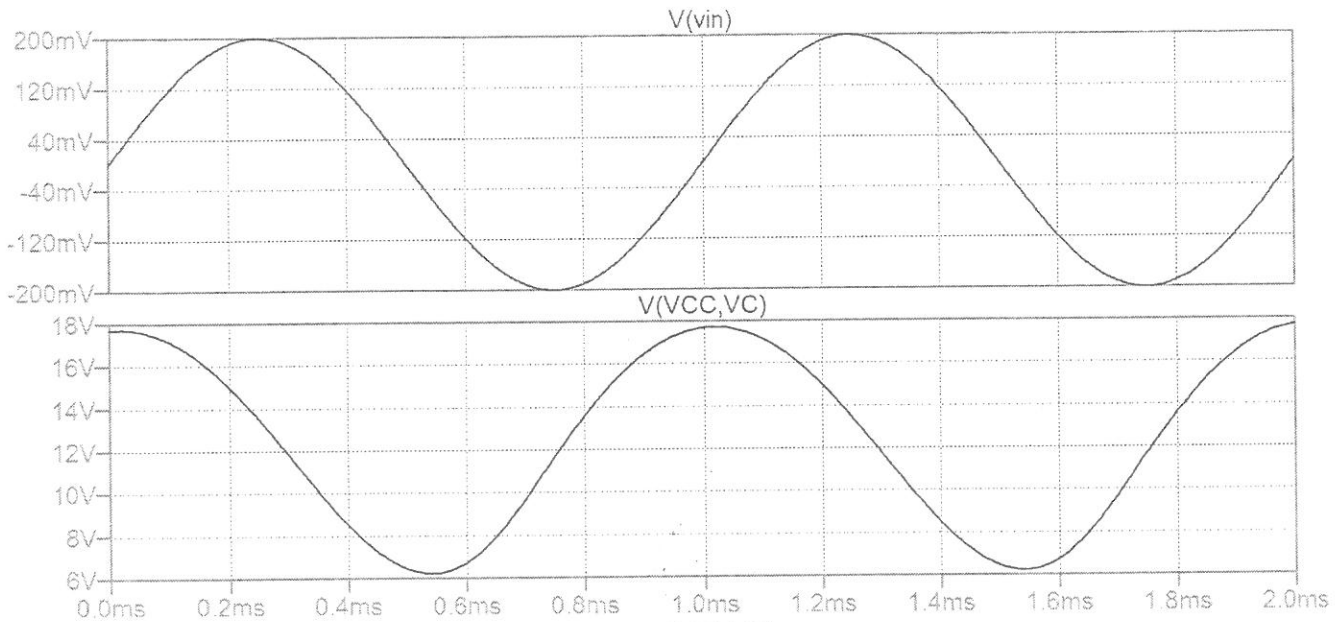


Figure-Q2(a)(ii)

- i. Identify the class of the power amplifier in Figure-Q2(a)(i). [2]
 - ii. Calculate the total DC power, P_{DC} , applied to the amplifier. [6]
 - iii. Calculate the estimated total AC power, P_{AC} , delivered to load R_{load} by the amplifier. [5]
 - iv. Calculate the power efficiency of the amplifier. [2]
 - v. State one advantage and one disadvantage of this type of power amplifier. [2]
- b. A class B power amplifier using common collector configuration, has a $\pm 25 V$ supply voltage, while its load resistance is 16Ω . A $20 V$ peak input AC voltage is supplied to this power amplifier. Assume ideal transistor operation, calculate
- i. its total input DC power, P_{DC} . [4]
 - ii. its output AC power, P_{AC} . [2]
 - iii. its power conversion efficiency in percentage. [2]

Question 3

- a. i. Most op-amps are powered in a dual supply mode. Explain the principal advantage to do so. [3]
- ii. State the output voltage expression of an op-amp, in terms of its two input voltages, V^+ and V^- , and its open-loop voltage gain, A_o . [2]
- iii. Explain output voltage saturation limit of an op-amp. [3]
- iv. Sketch the idealized voltage transfer characteristic, V_{out} versus $(V^+ - V^-)$, of an op-amp clearly. [3]
- b. For each of the following statement, state TRUE or FALSE.
- i. In ideal open-loop op-amp operation, the slightest non-zero value of $(V^+ - V^-)$ will drive its output voltage to saturation. [1]
- ii. When the output voltage of an op-amp lies between its power supply voltages, the op-amp is said to be operating in its saturation region. [1]
- iii. The input resistance of an op-amp is designed to be as low as possible so that negligible power dissipates in the op-amp. [1]
- iv. Applying negative feedback to an op-amp helps to reduce the overall voltage gain of the op-amp circuit. [1]
- v. Positive feedback should be entirely avoided in op-amp circuit design. [1]
- c. i. Design an op-amp circuit to implement the block diagram shown in Figure-Q3(c). [5]
- ii. Clearly sketch the idealized voltage transfer curve of the circuit. [4]

 


Figure-Q3(c)

Question 4

Figure-Q4 shows an active band pass filter adopting multiple feedback topology. The general voltage transfer function expression of the filter is given by,

$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{a_1 s}{s^2 + \left(\frac{\omega_o}{Q}\right) s + \omega_o^2}$$

 


Figure-Q4

- Explain the significant meaning of the negative sign shown in the given voltage transfer function expression. [2]
- Explain the meaning of the symbol “Q” and “ ω_o ” shown in the given voltage transfer function expression. [4]
- Relate “ a_1 ”, “Q” and “ ω_o ” to the passive components used in the filter. [10]
- By choosing $C_1 = 1 \text{ nF}$, determine the values for the remaining passive components so that the filter has a bandwidth of 4 kHz and a maximum voltage gain of 10 at 5 kHz. [9]

Question 5

- Figure-Q5(a)(i) shows a block diagram of an oscillator. Symbol A_v and β respectively represent the amplifier voltage gain and the system’s feedback factor. Figure-Q5(a)(ii) shows the output signal of the oscillator, measured when the circuit is first powered up.

 


Figure-Q5(a)(i)

 


Figure-Q5(a)(ii)

- i. State the family of the oscillator given in Figure-Q5(a)(i). [2]
- ii. Relate A_v and β for $t < 6 \text{ ms}$. [2]
- iii. Relate A_v and β for $t > 8 \text{ ms}$. [2]
- iv. State two existing examples of oscillator circuit that are built base on the configuration given in Figure-Q5(a)(i). [2]

b. Figure-Q5(b) shows an oscillator circuit which implements the circuit configuration as shown in Figure-Q5(a)(i). The circuit is at its steady-state condition.

 


Figure-Q5(b)

- i. By making use of the feedback network in Figure-Q5(b), show that output oscillating frequency of the circuit, in rad/s, is given by,

$$\omega_o = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}} \quad [6]$$

- ii. Show that, during steady-state, the magnitude expression of the voltage amplifier's gain, $|A_v|$, is given by,

$$|A_v| = \frac{C_1}{C_2} + \frac{R_2}{R_1} \quad [5]$$

- iii. Using as many equal-value components as possible, implement the circuit in Figure-Q5(b) to produce a signal oscillating with 5 kHz at steady-state condition. [6]

Question 6

- a. Figure-Q6(a) shows a common emitter amplifier circuit. Transistor Q_1 has the following values of hybrid parameters under its small-signal operating conditions: $h_{ie} = 1\text{ k}\Omega$, $h_{fe} = 100$, h_{oe} and h_{re} are negligible.

The amplifier has a voltage gain, $A_v = \frac{v_{out}}{v_{in}} = -10$ at frequency where the reactances of both C_1 and C_2 are negligible.

 


Figure-Q6(a)

- i. Draw the equivalent AC circuit model of the given amplifier in which its voltage gain, $A_v = -10$. [4]
 - ii. Calculate the required value of R_E . [5]
 - iii. Calculate the current gain, $A_i = \frac{i_{out}}{i_{in}}$. [6]
- b. i. State one advantage of a Schmitt Trigger Comparator as compared to an ordinary comparator circuit utilizing only an op-amp and one reference voltage. [2]
 - ii. Draw a non-inverting Schmitt Trigger Comparator that has positive upper and lower threshold points. The comparator is to be operated in single supply mode. [4]
 - iii. Design the circuit with threshold points set at 0.5 V and 2.5 V respectively, assume that the op-amp output saturates at 0V and 5V. [4]

~ The End ~