



FINAL
Examination Paper

(COVER PAGE)

Session : August 2017

Programme : Diploma in Electrical and Electronic Engineering (DEEI)

Course : EEE 2113: Electric Power Systems and Machines

Date of Examination : 7 December 2017 (Thursday)

Time : 2:00pm – 4:00pm Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Materials permitted :

Non-Programmable Scientific Calculator

Materials provided :

Nil

Examiner(s) :

Ken Kong Seng Kuok

Moderator :

Dr. Ooi Beng Lee

This paper consists of 7 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)
 EEE2113: ELECTRIC POWER SYSTEMS AND MACHINES
 FINAL EXAMINATIONS: AUGUST 2017 SESSION

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Question 1

- (a) List 3 characteristics of an ideal transformer. (6 marks)
- (b) Explain the reason that transformer is only applicable in A.C. circuit. (4 marks)
- (c) A 75 kVA, 4,800/240 V, 60 Hz, single-phase transformer has the following parameters (in Ω):

$R_{LS} = 0.0060$	$R_{HS} = 2.4880$	$R_{fe, HS} = 44,202$
$X_{LS} = 0.0121$	$X_{HS} = 4.8384$	$X_{M, HS} = 7798.6$

The transformer is operating in the step-down mode, delivering one-half rated load at rated voltage.

- i. Determine the equivalent impedance reflect to the primary side. (3 marks)
- ii. Determine the input impedance of the transformer that include the load and the parameters. Assume unity power factor. (3 marks)
- iii. Calculate the input impedance of the transformer with the load disconnected. (3 marks)
- iv. Calculate the exciting current flowing into transformer when the load is removed. (3 marks)
- v. Calculate the efficiency of the transformer when it is connected to the load. (3 marks)

Question 2

- (a) A shunt generator delivers 200 A at a terminal voltage of 250 V. The armature resistance and shunt field resistance are 0.02Ω and 50Ω respectively. The iron and friction losses amount to 1 kW.
- (i) **Calculate** the generated E.M.F. (4 marks)
 - (ii) **Estimate** the copper losses (3 marks)
 - (iii) **Calculate** the input power to the generator (3 marks)
 - (iv) **Estimate** the overall efficiency of the generator (3 marks)
- (b) A 30 kW, 250 V, D.C. shunt machine has an armature resistance of 0.06Ω and field resistance of 100Ω .
- (i) **Solve** for the total armature power developed when working as a motor taking 30 kW input. (6 marks)
 - (ii) **Solve** for the total armature power developed when working as a generator while delivering 30 kW of output. (6 marks)

Question 3

- (a) The load duration curve of a system is as shown in the following figure Q3. The system is supplied by three stations – a steam station, a run of river station and a reservoir hydro-electric station. The ratios of number of units supplied by the three stations are as below:

Steam	:	Run of river	:	Reservoir
7	:	4	:	1

The run of river station is capable of generating power continuously and works as a base load station. The reservoir plant works as a peak load station. **Estimate** the maximum demand on each station and also the load factor of each station.

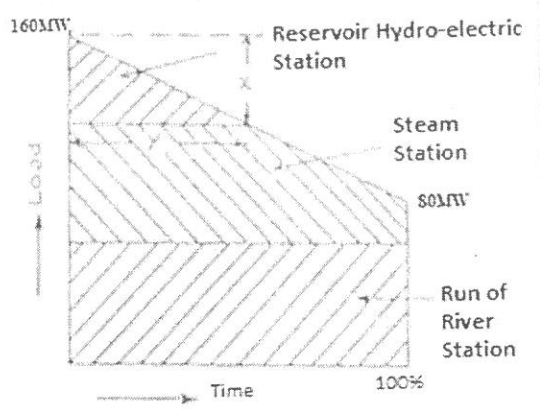


Figure Q3: Load duration curve

(25 marks)

Question 4

- (a) A 50 Hz, 3-phase transmission line of 100 km delivers 20 MW, 0.9 p.f. lagging, at 110 kV. The resistance and reactance of the line per phase are 0.2 Ω /km and 0.4 Ω /km respectively, while capacitive admittance is 2.5 μ S/km.

Using nominal T method:

- (i) **Calculate** sending end voltage and sending end current
 (ii) **Calculate** the efficiency of transmission

(10 marks)

(5 marks)

- (b) A single core cable of 0.5 km long has a core diameter of 0.5 cm and diameter under sheath of 2 cm. The relative permittivity of insulating material is 3.2. The supply voltage is 11 kV, 50 Hz. Take specific resistance of insulation as 5×10^{12} Ω /m, calculate the following:

- (i) **Determine** the capacitance of the cable, with $\epsilon_0 = 8.845 \times 10^{-12}$ Fm^{-1}
 (ii) **Estimate** the insulation resistance
 (iii) **Calculate** the charging current per conductor
 (iv) **Determine** the dielectric loss

(3 marks)

(3 marks)

(2 marks)

(2 marks)

Question 5

The two generating units are supplying to the grid as indicated in Figure Q5. The per unit voltage, current and impedance value are given as below.

$$I_1 = 1 \angle 0^\circ$$

$$I_2 = 0.8 \angle 0^\circ$$

$$V_1 = 1.05 \angle 10^\circ$$

$$V_2 = 1.07 \angle 15^\circ$$

$$Z_1 = 0.05 + j0.2$$

$$Z_2 = 0.06 + j0.3$$

$$Z_3 = 0.06 + j0.4$$

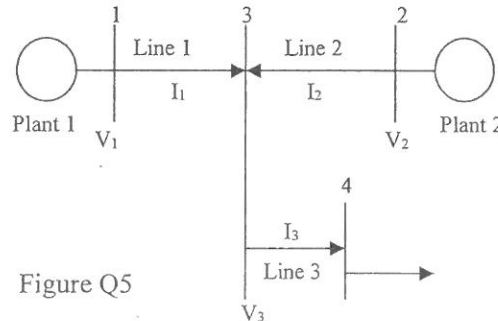


Figure Q5

- (i) **Determine** the system line coefficients associated with Line 1, Line 2 and Line 3. (15 marks)
- (ii) **Calculate** the penalty factor associated with each Plant (generating unit). (10 marks)

Question 6

- (a) A single core cable of conductor 1.8cm and lead sheath of diameter 6.3cm is to be used on a 66kV(line voltage), 3 phase system. There are two inter-sheaths of diameter 3.3cm and 4.8cm are introduced between the core and lead sheath. **Calculate** the voltages on the inter sheaths if the maximum stress in the layers is the same. (15 marks)
- (b) A 33 kV single core cable in a single-phase system has a conductor diameter of 1 cm and a sheath of inside diameter of 4 cm. **Determine** the maximum and minimum stress in the insulation. (10 marks)

Summary of Equations:

D.C. Machines

$$V_T = E_a + I_a R_{acir}$$

(motor voltage and emf relationship)

$$E_a = V_T + I_a R_{acir}$$

(generator voltage and emf relationship)

$$P_{mech} = V_T I_a - I_a^2 R_{acir}$$

mechanical power

$$T_D = \frac{9.55 P_{mech}}{n}$$

developed torque

$$\eta = \frac{P_{out}}{P_{input}}$$

machine efficiency

Transformers

$$a = \frac{N_{HS}}{N_{LS}} \approx \frac{V_{HS}}{V_{LS}}$$

turns ratio

$$I_{HS} = \frac{1}{a} I_{LS}$$

(high side-low side current relationship)

$$Z_{eq,HS} = R_{HS} + a^2 R_{LS} + j(X_{HS} + a^2 X_{LS})$$

impedance referred to high side

$$Z_{eq,LS} = \frac{1}{a^2} R_{HS} + R_{LS} + j\left(\frac{1}{a^2} X_{HS} + X_{LS}\right)$$

impedance referred to low side

$$Z_{in,HS} = Z_{eq,HS} + a^2 Z_{load}$$

input impedance (referred to high side)

Load Study

$$\text{average demand}(W) = \frac{\text{total energy demand}(W \cdot \text{hr})}{\text{total time}(hr)}$$

$$\text{load factor} = \frac{\text{average demand}(W)}{\text{maximum demand}(W)}$$

$$\text{demand factor} = \frac{\text{maximum demand}(W)}{\text{total connected load}(W)}$$

$$\text{diversity factor} = \frac{\text{sum of individual maximum demand}(W)}{\text{maximum demand on power station}(W)}$$

$$\text{plant capacity factor(plant factor)} = \frac{\text{average demand on the plant}(W)}{\text{total plant capacity}(W)}$$

$$\text{plant use factor(utilization factor)} = \frac{\text{actual energy produced}(W \cdot \text{hr})}{\text{plant capacity}(W) \times \text{total time}(hr)}$$

Per Unit System

$$Z_{pu(new)} = Z_{pu(old)} \times \left(\frac{V_{b(old)}}{V_{b(new)}}\right)^2 \times \frac{VA_{base(new)}}{VA_{base(old)}}$$

(changing per unit value from one base

reference to another base reference)

Cable Parameters

$$L = 2 \times 10^{-7} \ln\left(\frac{GMD}{GMR_L}\right) \text{ (H/m)}$$

(general per unit length inductance)

$$C = \frac{2\pi\epsilon}{\ln\left(\frac{GMD}{GMR_C}\right)} \text{ (F/m)}$$

(general per unit length capacitance)

Cable Grading

$$g = \frac{V_{12}}{x \ln\left(\frac{D_2}{D_1}\right)}$$

(dielectric stress)

$$V_n = g_{max} r_{n-1} \ln\left(\frac{r_n}{r_{n-1}}\right); n = 1, 2, 3 \dots$$

(voltage distribution)

Optimal Dispatch

$$\lambda = \frac{P_D + \sum_{i=1}^n \frac{\beta_i}{2\gamma_i}}{\sum_{i=1}^n \frac{1}{\gamma_i}}$$

(incremental cost)

$$P_i = \frac{\lambda - \beta_i}{2\gamma_i}$$

(power output)

Voltage Control Method

$$t_s = \sqrt{\frac{\frac{|V_1|}{|V_2|}}{1 - \frac{R P + X Q}{|V_1||V_2|}}}$$

ratio)

(tap-changing transformer adjustment

