



FINAL
Examination Paper
(COVER PAGE)

Session : April 2016

Programme : Diploma in Electrical and Electronic Engineering (DEEI)

Course : EEE 1105: Circuit Theory & Electronic Devices

Date of Examination : 2 August 2016, Tuesday

Time : 8.00am – 10.00am

Duration : 2 Hours Reading Time : Nil

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

IMPORTANT NOTE : THIS PAPER SHOULD NOT BE TAKEN OUT OF THE EXAMINATION HALL

Materials Permitted : Non-Programmable Scientific Calculator

Materials Provided : Answer Booklet

Examiner(s) : Ms. Shalyn Lim Sheue Hui

Moderator : Mr. Kevin Tan

This paper consists of 13 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING (DEEI)
 EEE 1105: CIRCUIT THEORY & ELECTRONIC DEVICES
 FINAL EXAMINATION: APRIL 2016 SESSION

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Question 1

(a) With reference to Figure Q1(a), calculate

- (i) the total resistance. (3 marks)
- (ii) the current, I . (2 marks)
- (iii) the currents, I_8 . (4 marks)

 


Figure Q1(a)

- (b) Given the voltmeter reading $V = 27\text{ V}$ in Figure Q1 (b) (i). Is the network operating properly? not, what could be the cause of the incorrect reading? (4 marks)

 


Figure Q1(b)

- (c) With reference to Figure Q1(c). Calculate voltage drop across 4Ω resistor using *Nodal Analysis*. (5 marks)

 


Figure Q1(c)

- (d) Calculate the maximum power transfer to R for the network shown in Figure Q1(d) (7 marks)

 


Figure Q1(d)

Question 2

- (a) For the following pairs of voltages and currents, indicate whether the element involved is a capacitor, an inductor, or a resistor, and the value of C , L or R if sufficient data are given

$$v = 550 \sin(377t + 50^\circ)$$

$$i = 11 \sin(377t - 40^\circ)$$

(3 marks)

- (b) An electrical system is rated 10 kVA, 200 V at a 0.5 leading power factor.

- (i) Determine the impedance of the system in complex form.

(3 marks)

- (ii) Find the average power delivered to the system.

(2 marks)

- (c) For the network of Figure Q2(c), given the rms of the supply voltage is $100 \angle 0^\circ$ V determine

[Note: answer in polar form]

- (i) the total admittance Y_T .

(4 marks)

- (ii) the voltage V_1 and V_2 .

(4 marks)

- (iii) the current I_3 .

(3 marks)

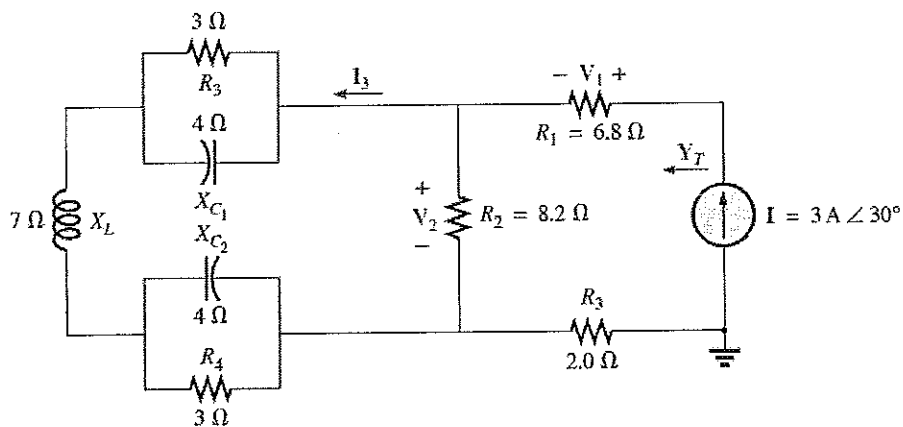


Figure Q2(c)

(d) Find the element or elements that must be in the closed container in Figure Q2(d) to satisfy the following conditions in (I) and (II).

- (I) Average power to the circuit = 3000 W.
- (II) Circuit has a lagging power factor.

(6 marks)

 


Figure Q2(d).

Question 3

(a) By using a diagram with the **detail label** of electric field and charges, explain the process of forming the depletion region in P-N junction. (5 marks)

(b) The circuit as shown in Figure Q3 (b) contains two silicon diodes D1 and D2. Calculate the values of their respective currents, I_1 , I_2 and I_3 . (5 marks)

 


Figure Q3(b)

- (c) Figure Q3 (c) shows the full wave rectifier circuit with the input sine wave.
- (i) Calculate the average output voltage, V_{AVG} . (4 marks)
 - (ii) Determine the value of PIV. (2 marks)
 - (iii) Sketch the output voltage at R_L with proper labeling. (2 marks)
 - (iv) Calculate the average diode current. (3 marks)

 


Figure Q3(c)

- (d) Sketch V_o for the network of Figure Q3(d) and determine the average output current. (5 marks)

 


Figure Q3(d)

Question 4

- (a) Using the load line analysis sketch and label the operating regions of the BJT. Why the setting of Q-point (dc operating point) is important? (7 marks)

- (b) Determine I_B, I_C and V_{CE} for the network shown in Figure 4(b) with $\beta=50$ (5 marks)

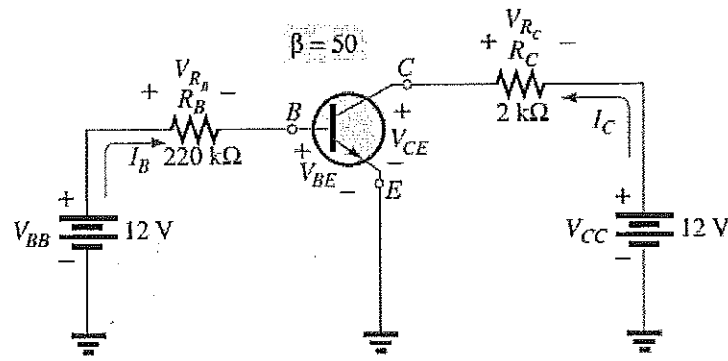


Figure 4(b)

(c) Given the emitter-bias configuration network of Figure Q4(c) with the given V_B and V_{BE} and the approximation $I_C \approx I_E$ is often applied to transistor networks.

(i) Determine V_E and I_E . (4 marks)

(ii) Calculate V_1 . (3 marks)

(iii) Determine V_{BC} . (4 marks)

(iv) Calculate V_{CE} . (2 marks)



Figure Q4(c)

Question 5

- (a) What are the advantages and disadvantages of FET compare to BJT. (4 marks)
- (b) The specifications of the n-channel E-MOSFET are given as: $V_{GS(Th)} = 4 \text{ V}$ and $I_{D(on)} = 4 \text{ mA}$ at $V_{GS(on)} = 6 \text{ V}$, determine k and write the general expression for the drain current, I_D . Sketch the transfer characteristics for this device. (6 marks)
- (c) For the FET as shown in Figure Q5(c) , calculate
- (i) the voltages V_G and V_S . (4 marks)
 - (ii) the currents I_1 , I_2 , I_D and I_S . (6 marks)
 - (iii) the V_{DS} and V_{DG} (5 marks)

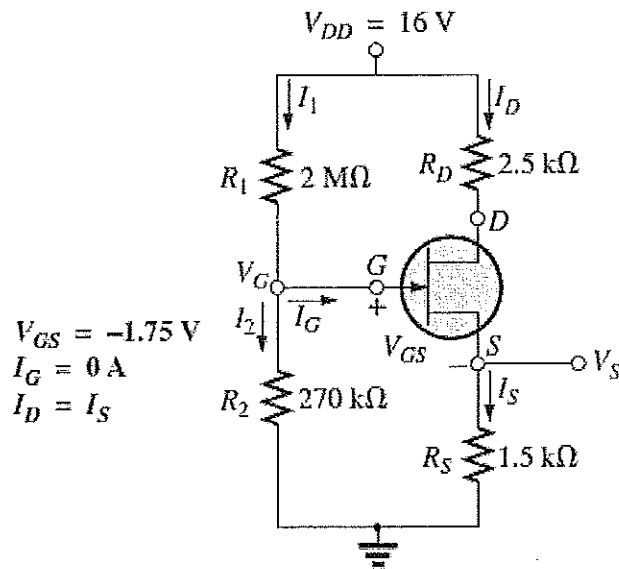


Figure Q5(c)

Question 6

(a) Refer to the circuit shown in Figure Q6 (a), find

(i) the currents I_2 , I_6 , and I_8 .

(7 marks)

(ii) the voltages V_4 and V_8 .

(4 marks)

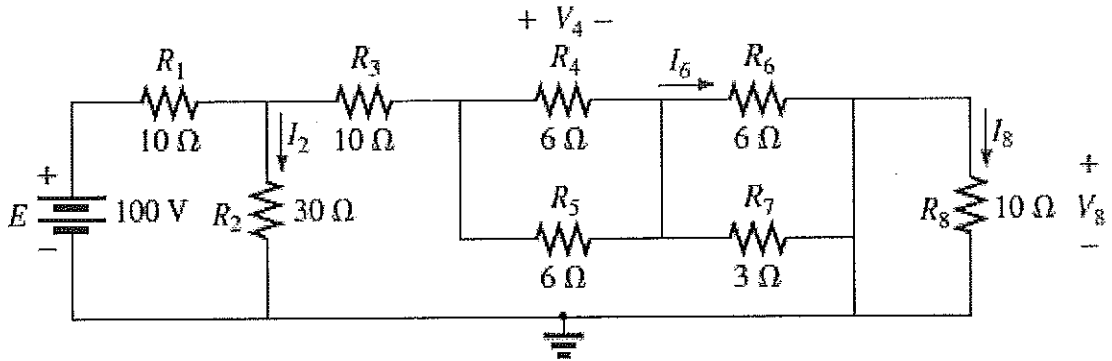


Figure Q6(a)

(b) Find the Norton equivalent circuit for the shaded area of the network to the left of a-b in Figure Q6(b).

(6 marks)

 


Figure Q6(b)

(c) The biasing circuit of Figure Q6 (c) has current gain $\beta = 200$. Assume $V_{BE} = 0.7$ V.

- (i) Calculate the quiescent operating point. (5 marks)
- (ii) Sketch the load line, properly labeling the saturation and cut-off points (3 marks)

 


Figure Q6(c)

-THE END-

EEE1105(F)APRIL16Shalyn Lim 28/06/16

