



**FINAL  
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : April 2020

Programme : Diploma in Electrical & Electronic Engineering (DEEI)

Course : EEE2101: Introduction to Digital Electronics

Date of Examination : 4 August 2020 (Tuesday)

Time : 2.00pm – 5.00pm Reading Time : Nil

Duration : 3 Hours

**Special Instructions :**

This paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry equal marks.

Material permitted : Nil

Materials provided : Nil

Examiner(s) : Mr Steven Khoo Boo Tap

Chief Moderator : Mr Chan Tse Wei

*This paper consists of 7 printed pages, including the cover page*

## INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)  
 EEE2101: INTRODUCTION TO DIGITAL ELECTRONICS  
 FINAL ALTERNATIVE ASSESSMENT: APRIL 2020 SESSION

Instructions: This paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry equal marks.

**Question 1**

- (a) Present the following Boolean expression using Karnaugh Map and/or Boolean algebra to the most simplified form:
- (i)  $F_1(X, Y, Z) = (X + Y + Z)(X + \bar{Y} + Z)(\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})$  to the simplest POS form. (3 marks)
- (ii)  $F_2(A, B, C, D) = \sum m(0,1,2,5,8,9) + d(10,11,12,13,14,15)$  to the minimum gates implementation. State the number of minimum gates used. (4 marks)
- (iii)  $F_3(K, L, M, N) = \prod M(1,5,7,11,12,14) \cdot \prod d(3,9)$  to the minimum gates implementation. State the number of minimum gates used. (5 marks)
- (b) Produce the simplest Boolean expressions for Y and Z in Figure 1(b) and interpret the expression to minimum 2-input NAND gate implementation only. State the minimum number of NAND gates and 7400 ICs (Integrated Circuits) used for the design. Show working clearly.

 


Figure 1(b)

- (c) Solve the numbering system transformation of  $[161.328125_{10} - 101.11_8 + FA.DE_{16}]$  to hexadecimal equivalent with 2 hexadecimal points accuracy. Show all workings clearly. (5 marks)

**Question 2**

- (a) Figure 2(a) shows the logic circuit diagram of an asynchronous counter, which uses positive edge-triggered T flip-flops with labelling of  $Q_A Q_B Q_C$  where  $Q_C$  is MSB and  $Q_A$  is LSB.

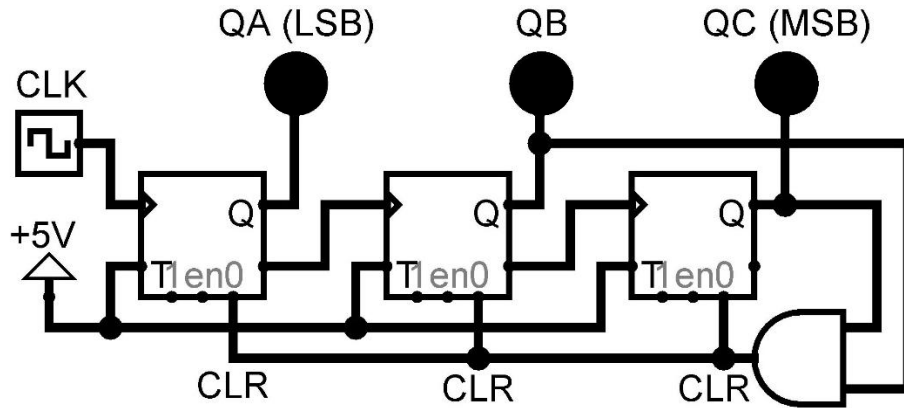


Figure 2(a)

- (i) Verify the counter operation whether the logic circuit of Figure 2(a) is working as an up counter or down counter. Also, state the modulus and function of this counter. (5 marks)
- (ii) Show the outputs,  $Q_A$ ,  $Q_B$ ,  $Q_C$  timing diagrams of Figure 2(a) with proper labelling for this counter. (5 marks)
- (b) Produce a synchronous 3-bit up/down counter using positive edge-triggered D flip-flop for MSB, JK flip-flop for second bit and SR flip-flop for LSB. Assume  $D_A$  is the MSB input,  $J_B$  &  $K_B$  are the next flip-flop inputs and  $S_C$  &  $R_C$  are the LSB inputs. Assume all unused states as don't care if applicable.

Input Z will be used as the up/down control. The counter will count from  $0 \Rightarrow 1 \Rightarrow 3 \Rightarrow 2 \Rightarrow 6 \Rightarrow 7 \Rightarrow 5 \Rightarrow 4 \Rightarrow 0$  when input,  $Z = 0$  and  $0 \Rightarrow 4 \Rightarrow 5 \Rightarrow 7 \Rightarrow 6 \Rightarrow 2 \Rightarrow 3 \Rightarrow 1 \Rightarrow 0$  when input,  $Z = 1$  as shown below in Figure 2(c). Flip-flop  $D_A$  has output  $Q_A$ , flip-flop  $J_B K_B$  has output  $Q_B$  and flip-flop  $S_C R_C$  has output  $Q_C$ . Provide proper labelling for the designed logic circuit. Show all workings clearly. Use the flip-flop excitation tables provide in Table 2(b).

Table 2(b)

Outputs		Inputs	
$Q_n$	$Q_{n+1}$	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

Outputs		Inputs	
$Q_n$	$Q_{n+1}$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Outputs		Input
$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

Outputs		Input
$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

$Q_n$ : Present State

$Q_{n+1}$ : Next State

- (i) Prepare the transition table/next state table for the up/down counter. (4 marks)
- (ii) Produce the simplest Boolean expressions for  $D_A$ ,  $J_B$ ,  $K_B$ ,  $S_C$  and  $R_C$  inputs using Karnaugh map and/or Boolean algebra. (5 marks)
- (iii) Construct the logic circuit diagram for the simplified Boolean expressions obtained in part (b)(ii) using D, JK, SR flip-flops and other logic gates with proper labelling. (6 marks)

 


Figure 2(c)

**Question 3**

- (a) Solve the numbering system transformation of  $[2020.02_8 \times 20.25_{10}]$  to hexadecimal equivalent with 2 hexadecimal points accuracy. Show all workings clearly. (5 marks)
- (b) Table 3(b) shows a portion of hex NOT gates (DM7404) datasheet. Compute the following parameters from this datasheet, show all working clearly:
  - (i) Power dissipation,  $P_{D(max)}$  on a DM7404 IC when the output condition is as shown in Figure 3(b). Assume that the  $V_{CC}$  used is 5.5V. (6 marks)

 


Figure 3(b)

(ii) Fan-out, a gate can safely drive. (3 marks)

(iii) Noise Margin voltages,  $V_{NL}$  and  $V_{NH}$ . (3 marks)

Table 3(b)

**Recommended Operating Conditions**

Symbol	Parameter	DM5404			DM7404			Units
		Min	Nom	Max	Min	Nom	Max	
$V_{CC}$	Supply Voltage	4.5	5	5.5	4.75	5	5.25	V
$V_{IH}$	High Level Input Voltage	2			2			V
$V_{IL}$	Low Level Input Voltage			0.8			0.8	V
$I_{OH}$	High Level Output Current			-0.4			-0.4	mA
$I_{OL}$	Low Level Output Current			16			16	mA
$T_A$	Free Air Operating Temperature	-55		125	0		70	°C

**Electrical Characteristics**

over recommended operating free air temperature range (unless otherwise noted)

Symbol	Parameter	Conditions	Min	Typ (Note 2)	Max	Units
$V_I$	Input Clamp Voltage	$V_{CC} = \text{Min}, I_I = -12 \text{ mA}$			-1.5	V
$V_{OH}$	High Level Output Voltage	$V_{CC} = \text{Min}, I_{OH} = \text{Max}$ $V_{IL} = \text{Max}$	2.4	3.4		V
$V_{OL}$	Low Level Output Voltage	$V_{CC} = \text{Min}, I_{OL} = \text{Max}$ $V_{IH} = \text{Min}$		0.2	0.4	V
$I_I$	Input Current @ Max Input Voltage	$V_{CC} = \text{Max}, V_I = 5.5 \text{ V}$			1	mA
$I_{IH}$	High Level Input Current	$V_{CC} = \text{Max}, V_I = 2.4 \text{ V}$			40	$\mu\text{A}$
$I_{IL}$	Low Level Input Current	$V_{CC} = \text{Max}, V_I = 0.4 \text{ V}$			-1.6	mA
$I_{OS}$	Short Circuit Output Current	$V_{CC} = \text{Max}$ (Note 3)	DM54	-20	-55	mA
			DM74	-18	-55	
$I_{CCH}$	Supply Current with Outputs High	$V_{CC} = \text{Max}$		6	12	mA
$I_{CCL}$	Supply Current with Outputs Low	$V_{CC} = \text{Max}$		18	33	mA

(c) Table 3(c) shows the current ratings of TTL series logic gates. A 74F32 OR gate output is driving a few other TTL inputs as shown in Figure 3(c).

- (i) Discover through calculation whether there is a loading problem. (5 marks)

TTL Series	Output Drive		Input Loading	
	$I_{OH}$	$I_{OL}$	$I_{IH}$	$I_{IL}$
74	400 $\mu$ A	16mA	40 $\mu$ A	1.6mA
74S	1.0mA	20mA	50 $\mu$ A	2.0mA
74LS	400 $\mu$ A	8mA	20 $\mu$ A	400 $\mu$ A
74AS	2.0mA	20mA	200 $\mu$ A	2.0mA
74ALS	400 $\mu$ A	8mA	20 $\mu$ A	100 $\mu$ A
74F	1.0mA	20mA	20 $\mu$ A	600 $\mu$ A

Table 3(c)

- (ii) The 74F32 OR gate output needs to be used to drive some 74AS inputs in addition to the load inputs. Compute how many additional 74AS inputs could the output drive without being overloaded? (3 marks)

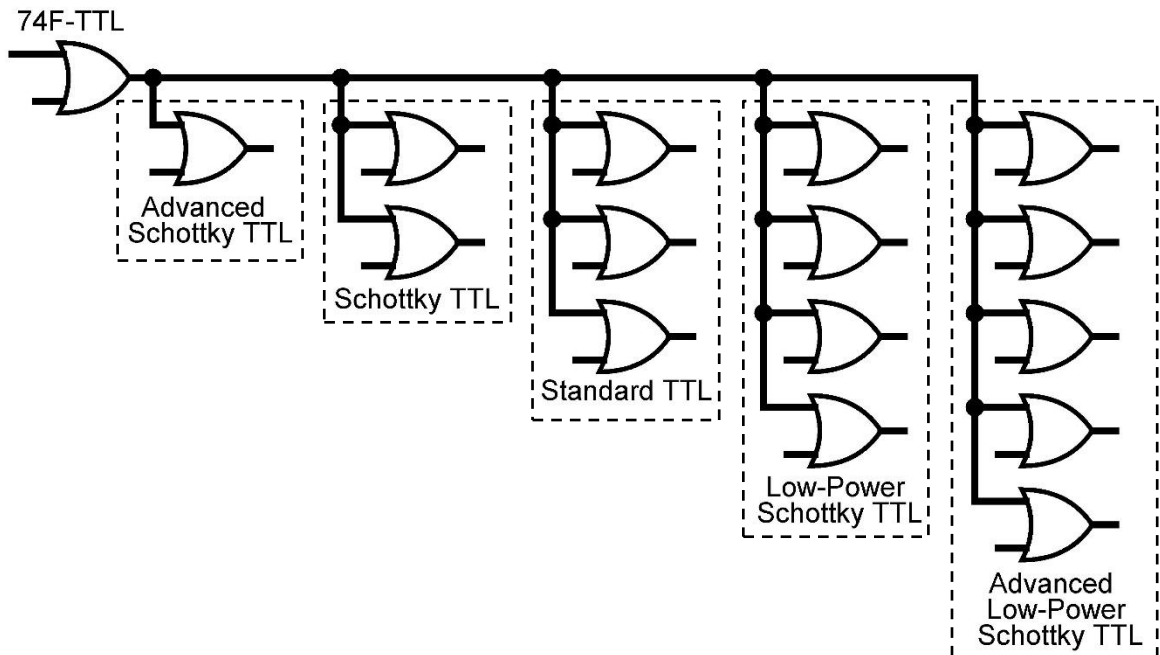


Figure 3(c)

**Question 4**

- (a) Compute the 2's complement number of  $-88.53125_{10}$  in signed binary numbering system. Assuming the binary system is 8-bit system with 8 binary points. Show all workings clearly. (5 marks)
- (b) Figure 4(b) shows a computer controlling the speed of a motor. The 0 to 2mA analog current from the DAC is amplified to produce motor speeds from 0 to 1000 rpm (revolutions per minute).
- (i) Compute how many bits should be used if the computer is to be able to produce a motor speed that is within 2 rpm of the desired speed? (5 marks)

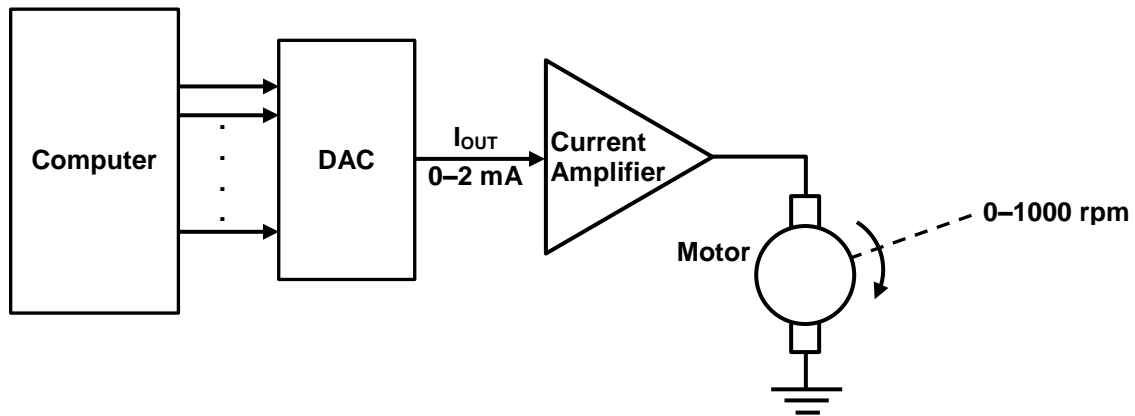


Figure 4(b)

- (ii) Using the number of bits obtained, compute how close to 250 rpm can the motor speed be adjusted? (5 marks)
- (c) An 10-bit digital ramp ADC with a 5V full-scale value output uses a clock frequency of 16MHz. Assume the number of steps is using  $2^n - 1$ . Compute the following values:-
- (i) the resolution and percentage of resolution. (4 marks)
- (ii) the digital output for an analog voltage of 2.020 V. (2 marks)
- (iii) the maximum and average conversion times. (4 marks)

– THE END –

EEE2101(F)/Apr2020/Steven Khoo/15/04/2020