



INTI
International College Penang

**FINAL
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : April 2022

Programme : Diploma In Electrical and Electronics Engineering (DEEI)

Course : EEE2112: Introduction to Power Electronics and Drivers

Date of Examination : 6 August 2022(Saturday)

Time : 12:00noon – 3:00pm Reading Time : Nil

Duration : 3 Hours

Special Instructions :

This paper consists of **FOUR (4)** questions. Answer all **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Material permitted : Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Khadijah Kamarulazizi

Chief Moderator : Richard Lai

This paper consists of 6 printed pages, including the cover page

INTI INTERNATIONAL COLLEGE PENANG
DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING (DEEI)
EEE2112: INTRODUCTION TO POWER ELECTRONICS AND DRIVERS
FINAL ALTERNATIVE ASSESSMENT: APRIL 2022 SESSION

Instructions: This paper consists of **FOUR (4)** questions. Answer all **FOUR (4)** questions. All questions carry equal marks.

Important notice: Computer software are **NOT** allowed in this exam except software to access the Question Paper and to submit the Answer Script. Answers are expected to be hand-written and required graph are to be manually plotted. Copy/paste and computer plotted graph will get zero marks.

Question 1

- (a) A single-phase 110 V, 500 W load is connected to single-phase 110 V, 50 Hz supply through a SCR as shown in Figure Q1(a). Find the RMS power delivered to the load for a SCR firing angle delays of 45° . [15]

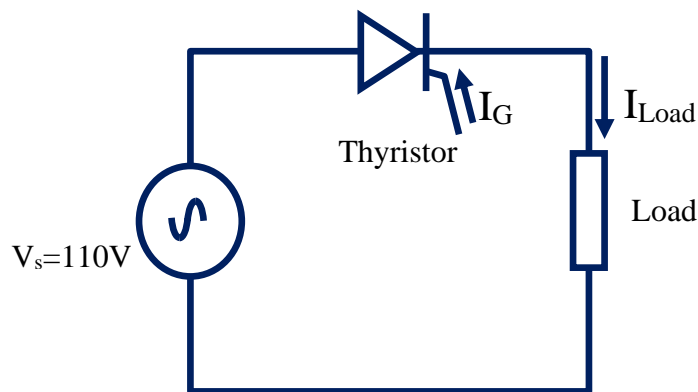



Figure Q1(a)

1.

(b) A single-phase bridge controlled rectifier as shown in Figure Q1(b), fed with single phase 230 V 50 Hz ac supply is used to control the dc supply. Assume the load consists of resistance $R_L=10\ \Omega$ and L is very large (infinite).

(i) Find the average output voltage and current given that the firing angle of the SCR is 30° and 210° . [6]

(ii) Sketch the load voltage if freewheeling diode connected across the load. [4]

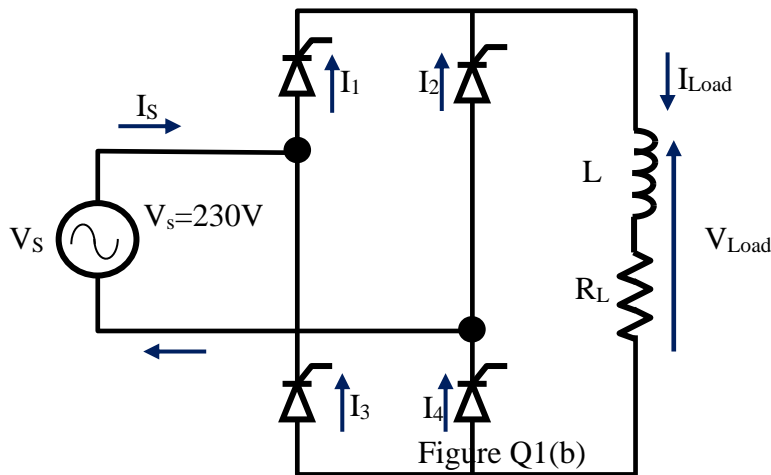

Question 2

A dc step-down converter connect to 48 V battery produces an output voltage of 18 V across a $10\ \Omega$ resistive load with output voltage ripple of 0.5 percent. Assume ideal components characteristic with the inductance 25% larger than the minimum value and switching frequency is 40 kHz, find:

(i) The duty ratio [2]

(ii) The value of the inductor. [4]

(iii) The value of the capacitor. [4]

(iv) The peak current and peak voltage at the inductor and capacitor respectively. [5]

(v) The rms current rating for the inductor. [3]

(vi) The voltage and current rating of the capacitor and inductor respectively.

Assume 100% safely margin. [4]

(vii) The voltage and current rating of the switching device. Assume 100% safely margin.

[3]

Question 3

A single phase full-bridge inverter has a resistive load of $R= 3 \Omega$ and the DC input voltage $V_{dc}= 24$

V. The switching elements used are power MOSFET. Find:

- (i) The total harmonic distortion THD. [3]
- (ii) The distortion factor DF up to 7th harmonics. [8]
- (iii) The harmonic factor and distortion factor of the 3rd harmonic only. [5]
- (iv) The real output power at the resistive load. [2]
- (v) The peak current at the load. [2]
- (vi) The average current at each switching element. [2]
- (vii) The switching frequency for each switching element is 100 Hz, find the frequency of the square wave generated by inverter if each MOSFET switch at 100hz [1]
- (viii) The new output power at the resistive load when an ideal 100 Hz low pass filter is connected to the inverter output. [2]

Question 4

A single phase full-wave AC chopper is shown in Figure Q4 below has a resistive load $R = 10 \Omega$ and the input voltage is $V_s = 120 \text{ V}_{\text{rms}}$, 50 Hz. The firing angles of thyristor T1 and T2 are equal: $\alpha_1 = \alpha_2 = 90^\circ$.

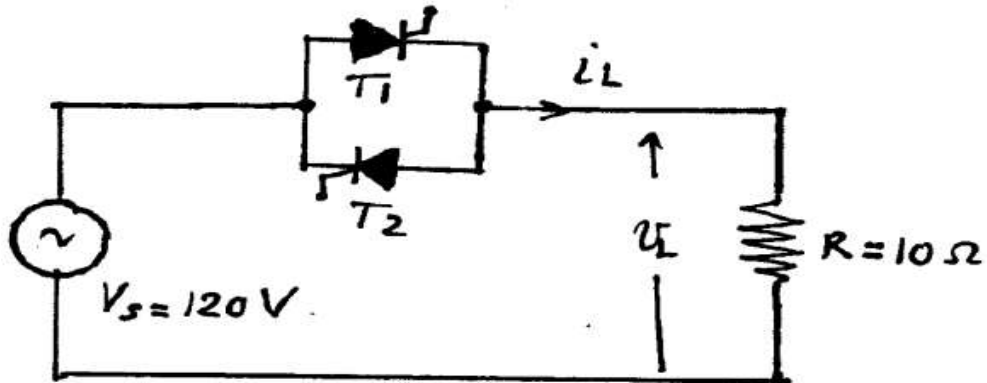


Figure Q4

- (a) (i) Sketch (draw and label) the output waveform at V_L and derive the $V_{L_{\text{r.m.s.}}}$ [5]
 (ii) Find the rms output voltage $V_{L_{\text{rms}}}$ [4]
- (b) Find the input power factor. [8]
- (c) Find the average and rms values of the thyristor current. [8]

--THE END--