

INTI
International College Penang
LAUREATE INTERNATIONAL UNIVERSITIES®

FINAL
Examination Paper

(COVER PAGE)

Session : AUGUST 2014

Programmes : Diploma in Electrical and Electronic Engineering (DEEL)

Course : ELECTRONIC DEVICES AND CIRCUIT THEORY 2 (EEE1103)

Date of Examination : December 13, 2014 (Saturday)

Time : 5.00pm – 7.00pm Reading Time: Nil

Duration : 2 Hours

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

Students are not allowed to remove this question paper from the examination venue.

Materials permitted :
Non-programmable scientific calculator

Materials provided:
NIL

Examiner(s) : Mr. Chan Tse Wei

Moderator : Dr. Ooi Beng Lee

This paper consists of 8 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)

**EEE1103 : ELECTRONIC DEVICES AND CIRCUIT THEORY 2
FINAL EXAMINATION : AUGUST 2014 SESSION**

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks. The marks allocated to each sub-question are shown in square brackets at the right-hand margin.

Question 1

a. Figure-Q1(a)(i) and (ii) shows two class-A power amplifiers.

 


Figure-Q1(a)(i)

 


Figure-Q1(a)(ii)

- i. Which power amplifier in Figure-Q1(a) has a higher power efficiency? [2]
 - ii. Qualitatively justify your answer in part (a)(i). [4]
 - iii. Sketch the respective AC load lines for each power amplifier in Figure-Q1(a). Assume that the transformer in Figure-Q1(a)(ii) has negligible wiring resistance. [6]
- b. The peak voltage and current swings of a power amplifier circuit are shown in Figure Q1(b). Calculate the output power and the power efficiency of the circuit. [6]

 


Figure-Q1(b)

- c. Illustrate in detail the power dissipation in a transistor using appropriate thermal analogy. [7]

Question 2

- a. i. Sketch the generic frequency response curve of a transistor based voltage amplifier, clearly showing its cutoff frequencies. [5]
 ii. If the amplifier system is configured as an audio amplifier system, what should be the theoretical cutoff frequencies of the system? [2]

- b. Figure Q2(b) shows a FET based amplifier circuit. The lower cutoff frequency of the amplifier circuit is to be set at $240Hz \pm 1\%$.

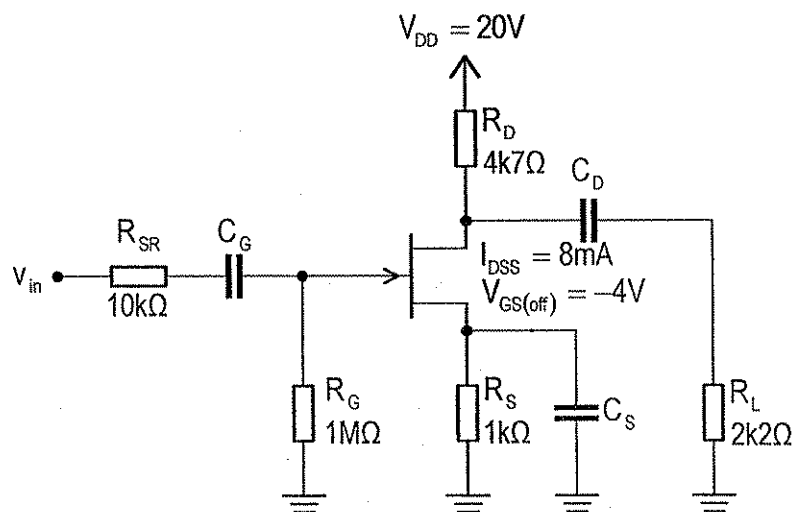


Figure-Q2(b)

- i. Draw the DC equivalent circuit for the amplifier in Figure-Q2(b). [2]
- ii. Hence, determine the transconductance (g_m) of the FET transistor at its operating point. [4]
- iii. With the transconductance obtained in part (b)(ii), draw the AC equivalent circuit for the amplifier in Figure-Q2(b). [3]
- iv. If the given cutoff frequency for the amplifier circuit is to be solely contributed by capacitor C_S in Figure-Q2(b), calculate the appropriate value for C_S . [5]
- v. If capacitors C_G and C_D in Figure-Q2(b) are to contribute a cutoff frequency which is a decade lower than 240Hz, calculate the appropriate value for these capacitors. [4]

Question 3

- a. Figure-Q3(a) shows an inverting amplifier circuit.

 


Figure-Q3(a)

- i. State the voltage at node- a in Figure-Q3(a). Why is the voltage as such? [2]
 - ii. What is the voltage gain of the circuit in Figure-Q3(a) if $R_1 = 2.4\text{k}\Omega$ and $R_2 = 36\text{k}\Omega$? [2]
 - iii. State two possibilities that can cause the output voltage in Figure-Q3(a) to saturate. For each given possibility, state the reason. [4]
 - iv. If V_{in} and the ground point connections in Figure-Q3(a) is interchanged, what is the voltage gain of the circuit? [4]
- b. Figure-Q3(b)(i) shows a non-inverting Schmitt Trigger Comparator and Figure-Q3(b)(ii) shows the voltage transfer curve of the comparator to be implemented. The op-amp used in the comparator circuit is assumed ideal
- i. Identify the upper and lower threshold points (UTP and LTP) of the design. [2]
 - ii. Show that the node voltage at the non-inverting input of the op-amp can be expressed as, [3]

$$V^+ = \frac{R_2 V_{in} \pm 12 R_1}{R_1 + R_2}$$

- iii. Show that, to implement the voltage transfer curve in Figure-Q3(b)(ii), $R_2 = 24R_1$. [6]
- iv. Determine the required value of V_{ref} in Figure-Q3(b)(i) if $R_1 = 1k\Omega$. [2]

 


Figure-Q3(b)(i)

 


Figure-Q3(b)(ii)

Question 4

- a. i. Explain how a low pass active filter and a high pass active filter may be utilized to form a band pass filter. [2]
- ii. State one design constrain of the band pass filter implemented in part (a)(i). [2]
- iii. State the general transfer function of the band pass filter implemented in part (a)(i) if only 1st order active filters are utilized. [4]
- iv. Draw the circuit diagram of the band pass filter implemented in part (a)(iii). [4]
- b. Figure-Q4(b) shows a second order active filter circuit that is commonly called as *universal filter*.
- i. Identify all the virtual ground points in the circuit and hence derive the voltage expression at node-a in terms of V_{out2} . [2]
- ii. By writing nodal equations at relevant virtual ground points, derive the voltage expressions for V_{out1} , V_{out2} and V_{out3} in terms of V_{in} , R and C . [8]
- iii. Hence, determine the three respective output functions of the filter circuit. [3]

 


Figure-Q4(b)

Question 5

- a.
 - i. Draw a schematic diagram of a square wave generator using only ONE (1) operational amplifier and some passive components. [3]
 - ii. State the oscillation frequency (f_o) expression of the generator in terms of the circuit elements drawn in part (a)(i). [2]
 - iii. Briefly elaborate the circuit operation to produce the desired square wave. [4]
 - iv. Suggest suitable circuit component values to produce an oscillation frequency of 10 kHz. [3]
- b. Figure-Q5(b) shows a block diagram of a harmonic oscillator.

 


Figure-Q5(b)

- i. If $\beta = -0.02$, what type of amplifier circuit should be chosen to implement A_v and what is the amplifier gain to sustain output oscillation? [4]
- ii. If $|A_v| = 30$ in Figure-Q5(b) due to component variations, how does it affect the output of [3]

the oscillator circuit?

- iii. State the two most probable root causes if the output oscillation saturates. [4]
- iv. State the two oscillator circuits that is implemented based on the block diagram in Figure-Q5(b). [2]

Question 6

- a. A dc voltage supply provides 60 V when the output is unloaded. When connected to full load, the output drops to 56 V. Calculate the value of the voltage regulation with reference to the full-load voltage in percentage. [4]

Figure-Q6(b) shows a pin-out diagram of an IC voltage regulator.

 


Figure-Q6(b)

- i. Under normal operating condition, what is the expected output voltage of the voltage regulator in Figure-Q6(b)? [2]
 - ii. The voltage regulator in Figure-Q6(b) has a minimum drop out voltage of 2V, what does that mean? [2]
 - iii. Draw the schematic diagram of a voltage regulator utilizing the one in Figure-Q6(b) so that a 5.7V regulated output voltage is obtained. [2]
- c. The nominal maximum output current for the IC voltage regulator in Figure-Q6(b) is approximately 1.0A. In order to support a load that draws more than 1.0A from the voltage regulator, the circuit in Figure-Q6(c) can be implemented. Explain the significant operation of the circuit in Figure-Q6(c). [5]

 


Figure-Q6(c)

d. Figure-Q6(d) shows an example of a voltage regulator circuit.

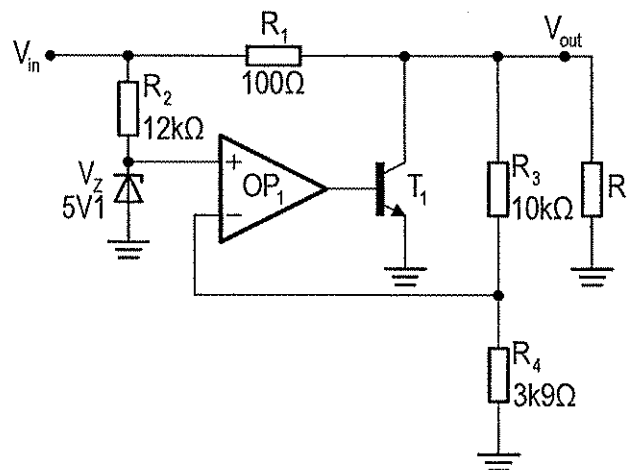


Figure-Q6(d)

- i. Assume that the output voltage of the regulator circuit in Figure-Q6(d) is perfectly regulated, determine the change in collector current if the input voltage changes by 1V. [3]
- ii. Determine the output voltage value that is being regulated in Figure-Q6(d). [3]
- iii. In Figure-Q6(d), if $V_m = 30\text{V}$ and the power rating of resistor R_1 is 1W, determine the lowest value for load resistor R_L that can be connected across the voltage regulator output. [4]

– THE END –