

INTI
International College Penang
LAUREATE INTERNATIONAL UNIVERSITIES®

FINAL
Examination Paper

(COVER PAGE)

Session : AUGUST 2014

Programmes : Diploma in Electrical and Electronic Engineering (DEEI)

Course : CIRCUIT THEORY AND ELECTRONIC DEVICES (EEE1105)

Date of Examination : December 12, 2014 (Friday)

Time : 5.00pm – 7.00pm Reading Time: Nil

Duration : 2 Hours

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

Students are not allowed to remove this question paper from the examination venue.

Materials permitted : Non-programmable scientific calculator

Materials provided: Worksheet for Q3(b)

Examiner(s) : Mr. Chan Tse Wei

Moderator : Dr. Cheah Kean Seng

This paper consists of 9 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)

EEE1105 : CIRCUIT THEORY AND ELECTRONIC DEVICES FINAL EXAMINATION : AUGUST 2014 SESSION

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks. The marks allocated to each sub-question are shown in square brackets at the right-hand margin.

Question 1

- a. Calculate the value and direction of the current flowing through the 40Ω resistor in the circuit shown in Figure-Q1 using Thevenin's Theorem. [8]

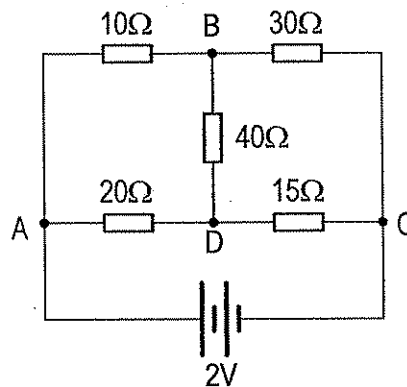


Figure-Q1

- b. Justify your answer in part (a) using Nodal Analysis. [8]
- c. Base on the effort in part (a) and part (b), comment on the advantage of Nodal Analysis as compared to Thevenin's Theorem. [4]
- d. Do Nodal Analysis and Thevenin's Theorem provide a direct approach to determine the total current drawn from the 2V supply voltage in Figure-Q1(a)? Explain your answer. [5]

Question 2

a. Figure-Q2(a) shows a sinusoidal current signal superimposed with a DC current component. Calculate,

- i. The DC current component of the signal. [2]
- ii. The frequency of the signal. [2]
- iii. The RMS value of the signal. Show the derivation of the formula used in the calculation. [6]

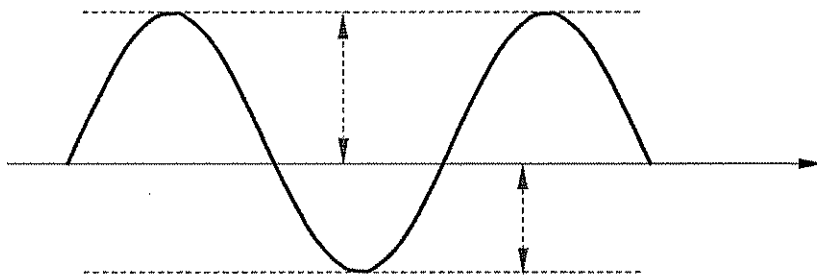


Figure-Q2(a)

b. A 15Ω resistor is connected in series with a coil of inductance 0.08H . The combined circuit is connected to a 240V , 50Hz supply. Calculate,

- i. The reactance of the coil. [2]
- ii. The impedance the circuit in polar form. [2]
- iii. The current flowing in the circuit in polar form. [2]
- iv. The power factor of the circuit. [2]
- v. The active power absorbed by the circuit. [2]

c. Convert the T-network in Figure-Q2(c) to its equivalent π -network. [5]

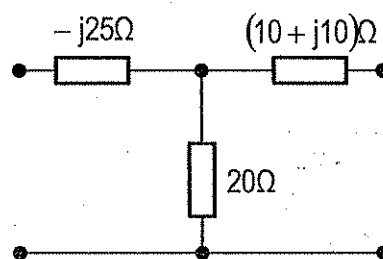


Figure-Q2(c)

Question 3

- a. The forward bias IV curve of a diode is as shown in Figure-Q3(a).

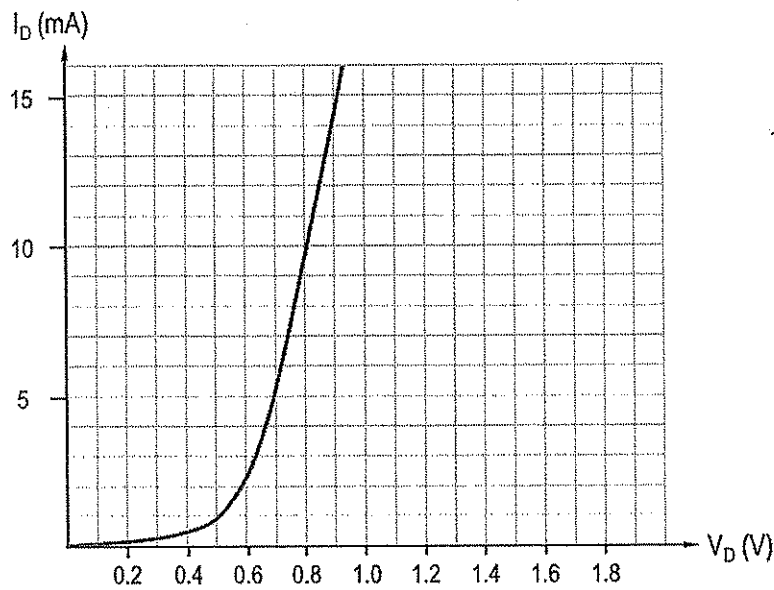


Figure-Q3(a)

- i. Approximate the knee voltage of the diode. [2]
 - ii. Calculate the diode's static resistance if 0.8V is applied across the diode. [3]
- b. Figure-Q3(b) shows a simple diode circuit in which the diode has an IV characteristic similar to the one shown in Figure-Q3(a).

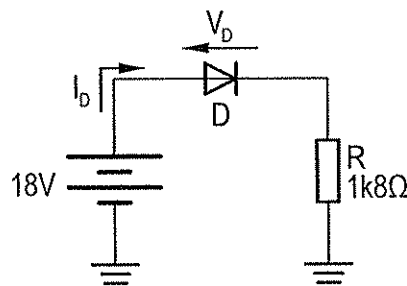


Figure-Q3(b)

- i. Write the circuit current expression, I_D in terms of V_D . [2]
- ii. Draw the DC load line of the circuit in Figure-Q3(b) on the accompanying worksheet. [4]
- iii. Hence, determine the quiescent current and voltage of the diode. [2]

- iv. If an AC voltage component of 0.1V peak is superimposed across the quiescent diode voltage in Figure-Q3(b), sketch the voltage waveform across resistor R , showing clearly its maximum and minimum voltage. [6]
- c. i. Figure-Q3(c) shows a piecewise model of the diode in part (a). Determine the value of V_{D0} and r_d . [4]
- ii. Base on the piecewise model in Figure-Q3(c), what is the diode current if 0.5V is applied across the diode? [2]

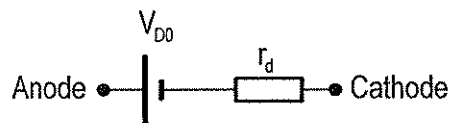


Figure-Q3(c)

Question 4

- a. Complete Table-Q4(a) by stating if the corresponding junctions should be forward or reverse biased for each of the listed BJT operating mode. Copy the table into your answer booklet. [6]

Mode of Operation	B-E Junction Biasing Condition	B-C Junction Biasing Condition
ON switch		
OFF switch		
Amplifying		

Table-Q4(a)

- b. A transistor with $\alpha = 0.98$ is biased so that $I_{BQ} = 0.1\text{mA}$. Calculate,
- i. I_{CQ} [4]
- ii. I_{EQ} [2]

c. Figure-Q4(b) shows a common BJT biasing circuit.

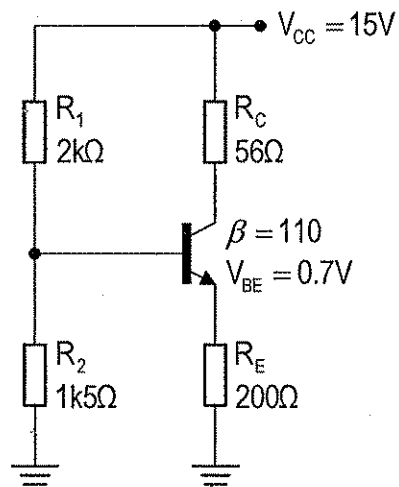
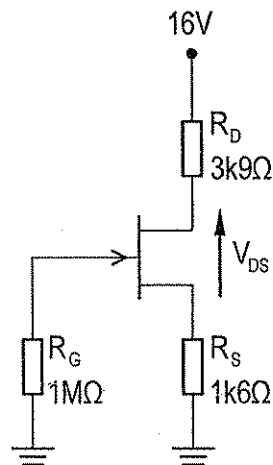


Figure-Q4(b)

- i. State the name of the biasing circuit. [2]
- ii. State the main advantage of the biasing circuit. [2]
- iii. Calculate the quiescent emitter current, I_{E_Q} of the circuit with the assumption that $I_{B_Q} \neq 0$ A. [6]
- iv. By taking into consideration that $I_{C_Q} \neq I_{E_Q}$, calculate V_{CE_Q} . [3]

Question 5

- a. i. Draw the respective symbols for the n-channel E-MOSFET and n-channel D-MOSFET. [4]
- ii. State ONE difference between E-MOSFET and D-MOSFET when the gates of both transistors are left unconnected. [2]
- b. An n-channel JFET has the following characteristics: $I_{DSS} = 10\text{mA}$, $V_{GS,off} = -7\text{V}$
- i. Explain the parameters I_{DSS} and $V_{GS,off}$ of a JFET. [4]
- ii. If -3V is applied across the gate-source terminals of the n-channel JFET, calculate the expected drain current flowing through the transistor? [3]
- iii. If 6mA is desired for the drain current, calculate the voltage that should be applied across the gate-source terminals. [3]
- iv. If the n-channel JFET is biased by the circuit shown in Figure-Q5(b), determine the value of V_{DSQ} . [9]

**Figure-Q5(b)**

Question 6

- a. For the network shown in Figure-Q6(a), the transistor has the following characteristics:
 $V_{GS_{off}} = -8V$ and $I_{DSS} = 8mA$.

Calculate,

- i. I_{D_Q} [6]
- ii. V_{GS_Q} [2]
- iii. V_{S_Q} [2]
- iv. V_{DS_Q} [3]

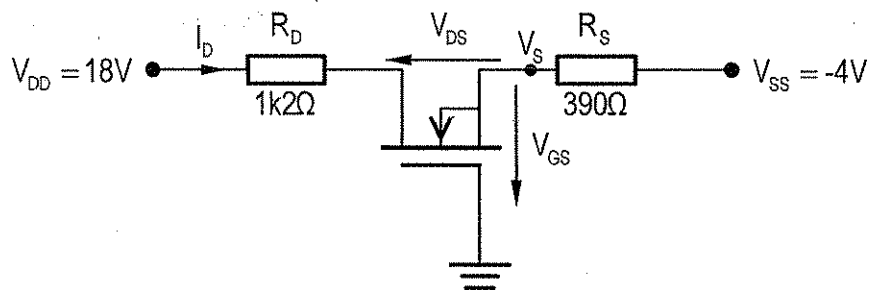


Figure-Q6(a)

- b. For the network shown in Figure-Q6(b), the transistor has the following characteristics:
 $V_{BE_Q} = 0.65V$ and $\beta = 120$.

Calculate,

- i. I_{B_Q} [4]
- ii. I_{C_Q} [2]
- iii. V_{CE_Q} [3]
- iv. V_{C_Q} [1]
- v. The current flowing through resistor R_E if resistor R_C is open-circuited. [2]

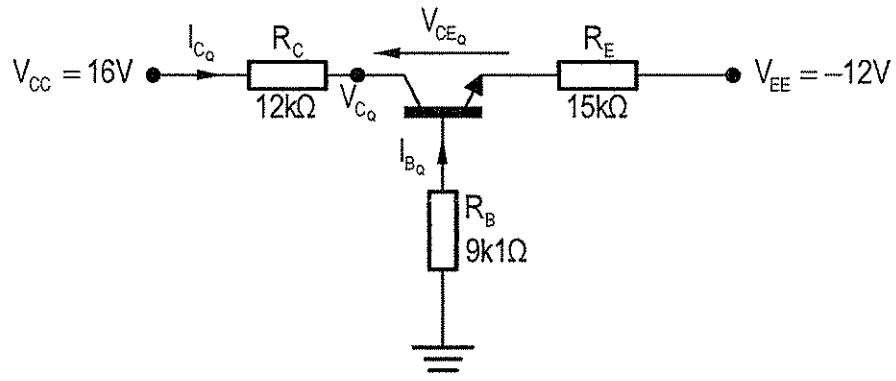


Figure-Q6(b)

– THE END –

Worksheet for Question 3(b)