



INTI
International College Penang

FINAL
Examination Paper

(COVER PAGE)

Session : August 2018

Programme : Diploma in Electrical and Electronic Engineering (DEEI)

Course : EEE 1105: Circuit Theory & Electronic Devices

Date of Examination : 11 December 2018 (Tuesday)

Time : 2:00pm – 4:00pm Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

IMPORTANT NOTE : THIS PAPER SHOULD NOT BE TAKEN OUT OF THE EXAMINATION HALL

Materials permitted : Non-Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Dr. Lee Zhi Hou

Moderator : Dr. Ooi Beng Lee

This paper consists of 11 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)
EEE1105: CIRCUIT THEORY & ELECTRONIC DEVICES
FINAL EXAMINATION: AUGUST 2018 SESSION

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Question 1 (25 marks)

- (a) For the circuit shown in Figure 1(a), find the value of voltage V_{ab} using voltage divider rule

(5 marks)

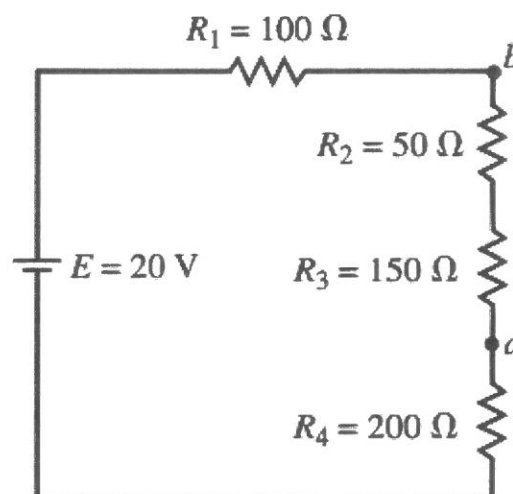


Figure 1(a)

(b) A circuit is arranged as shown in Figure 1(b). Determine :

- (i) R_T (equivalent resistance “seen” by the voltage source). (6 marks)
- (ii) the current I_1 . (2 marks)
- (iii) the current I_5 . (the current that flows through resistor R_5). (4 marks)

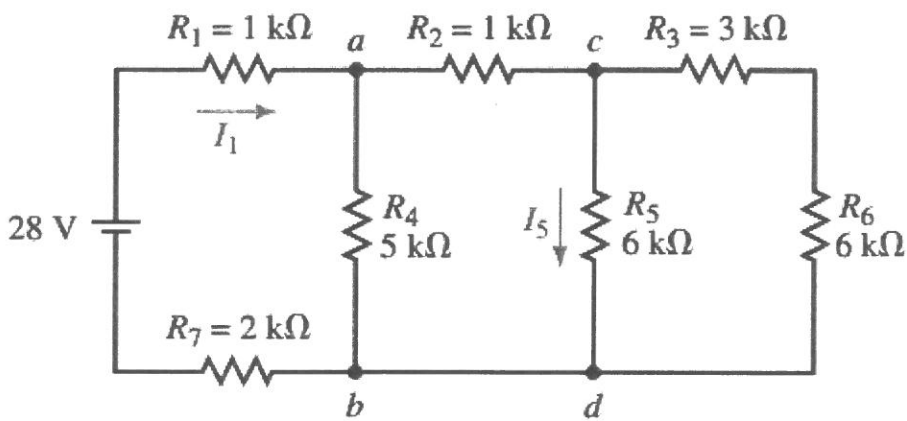


Figure 1(b)

(c) Using Superposition Theorem, calculate the voltage V_{ab} in Figure 1(c).

(8 marks)

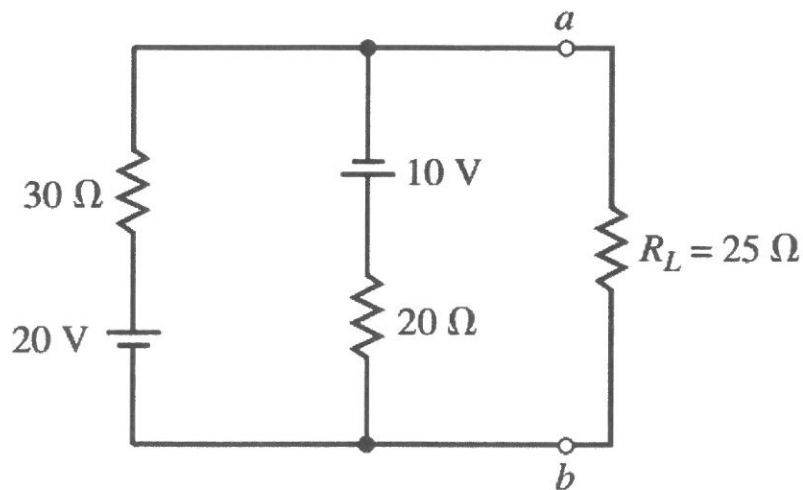


Figure 1(c)

Question 2 (25 marks)

(a) Refer to the circuit in Figure 2(a),

(i) find the Thevenin equivalent external to resistor R_L .

(8 marks)

(ii) use the Thevenin equivalent circuit to determine the value of the current I_L .

(4 marks)

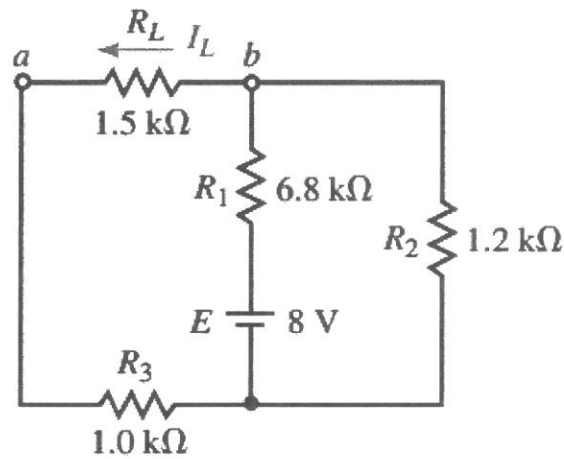


Figure 2(a)

(b) Write the nodal equations for the circuit in Figure 2(b) and then calculate the voltage V_{ab}

(13 marks)

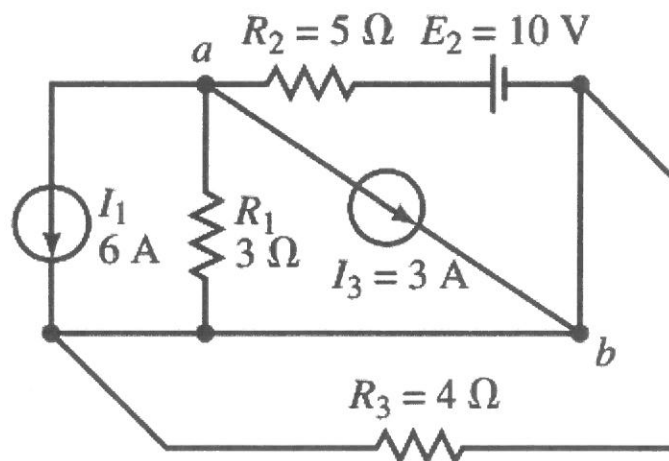


Figure 2(b)

Question 3 (25 marks)

- (a) Refer to the circuit in Figure 3(a), given that the total capacitance C_T is $20\mu\text{F}$, determine the value of capacitor C_x .

(4 marks)

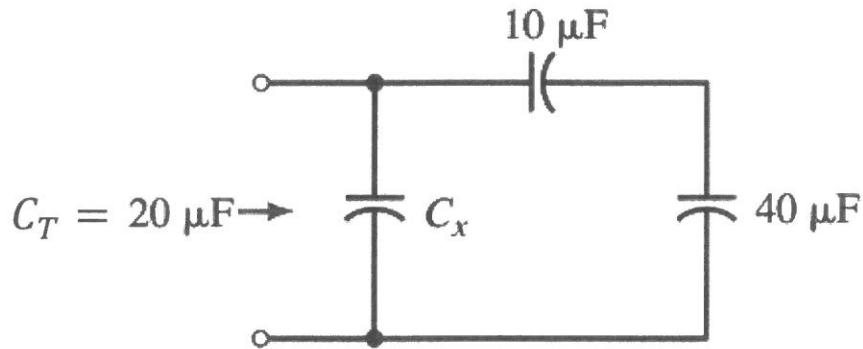


Figure 3(a)

- (b) The circuit in Figure 3(b) shows the alternating currents (AC) circuit for certain application.

- i) Determine the total impedance Z_T that is “seen” by the voltage source.

(8 marks)

- ii) Calculate each of the currents I_1 , I_2 and I_3 .

(6 marks)

- iii) Find the power factor and state the circuit is “lagging” or “leading”.

(3 marks)

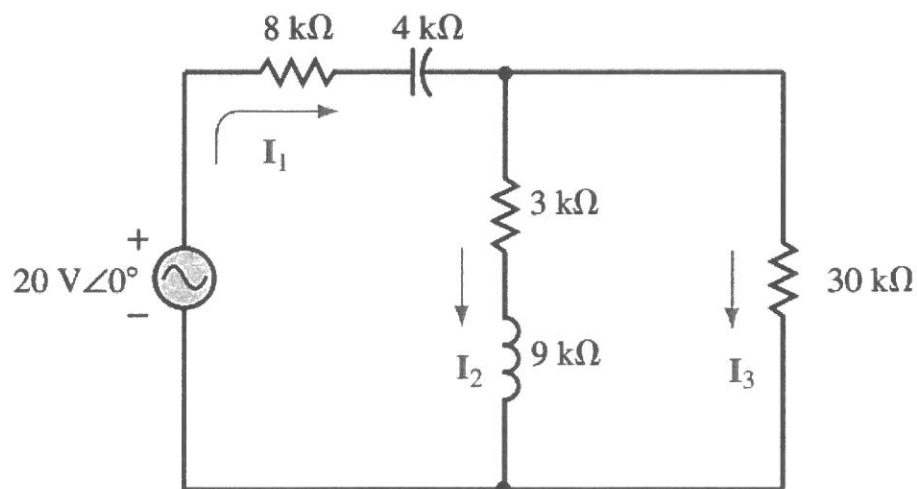


Figure 3(b)

(c) Figure 3(c) shows a series resonant circuit.

- (i) Determine the resonant frequency of the circuit in **radians per seconds** and **Hertz (Hz)**.

(4 marks)

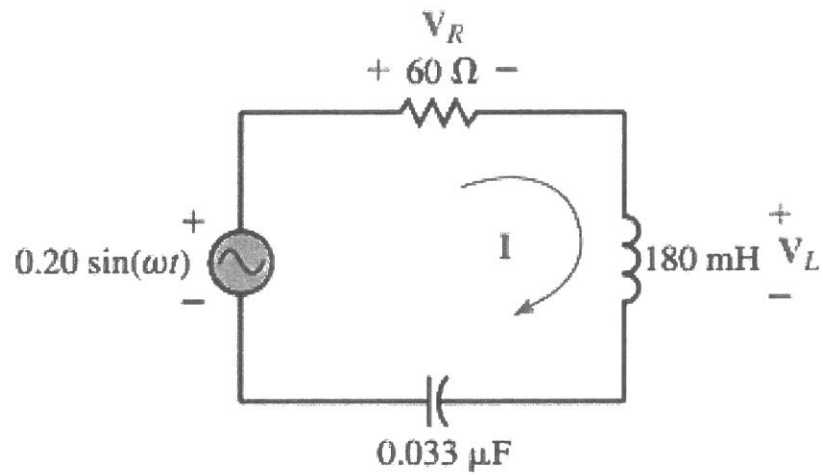


Figure 3(c)

Question 4 (25 marks)

(a) Figure 4(a) illustrates a silicon diode circuit, by assuming that the forward bias voltage of the silicon diode $V_D = 0.7\text{ V}$, determine:

(i) $V_{10\Omega}$ (the voltage dropped across resistor $10\ \Omega$) (2 marks)

(ii) $V_{20\Omega}$ (the voltage dropped across resistor $20\ \Omega$) (2 marks)

(iii) the current I . (4 marks)

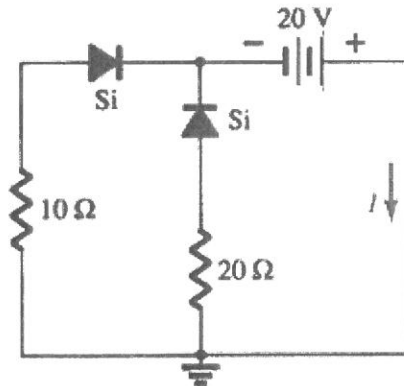


Figure 4(a)

(b) Figure 4(b) shows an ideal diode circuit. Sketch the output voltage v_o for the given input voltage v_i as shown. Assume that $5RC \gg \frac{T}{2}$.

(10 marks)

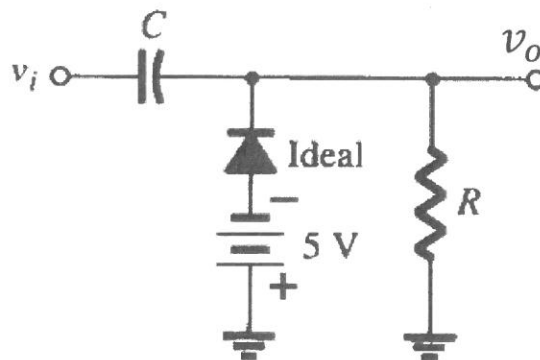
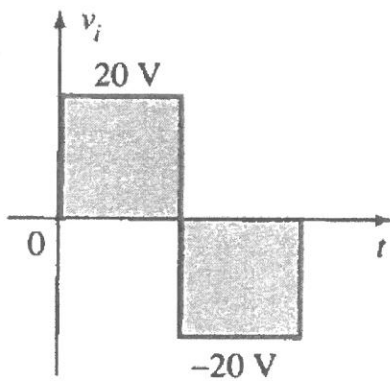


Figure 4(b)

(c) The circuit in Figure 4(c) illustrate the application of Zener diode. Given the Zener voltage V_z is 7 V and the Load Resistor R_L is 250 Ω ,

(i) Find the voltage V_L and current I_L .

(4 marks)

(ii) Determine the current I_R .

(3 marks)

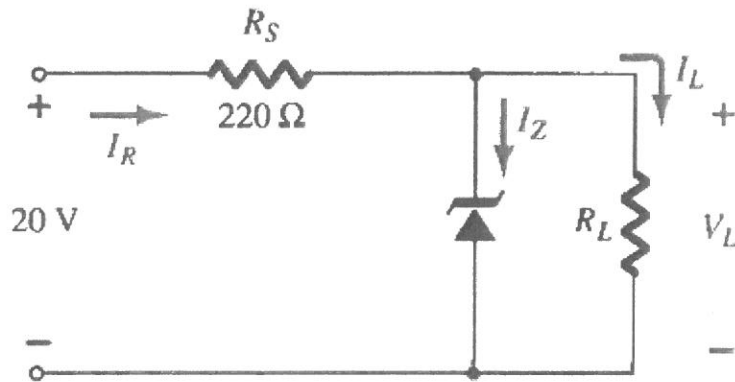


Figure 4(c)

Question 5 (25 marks)

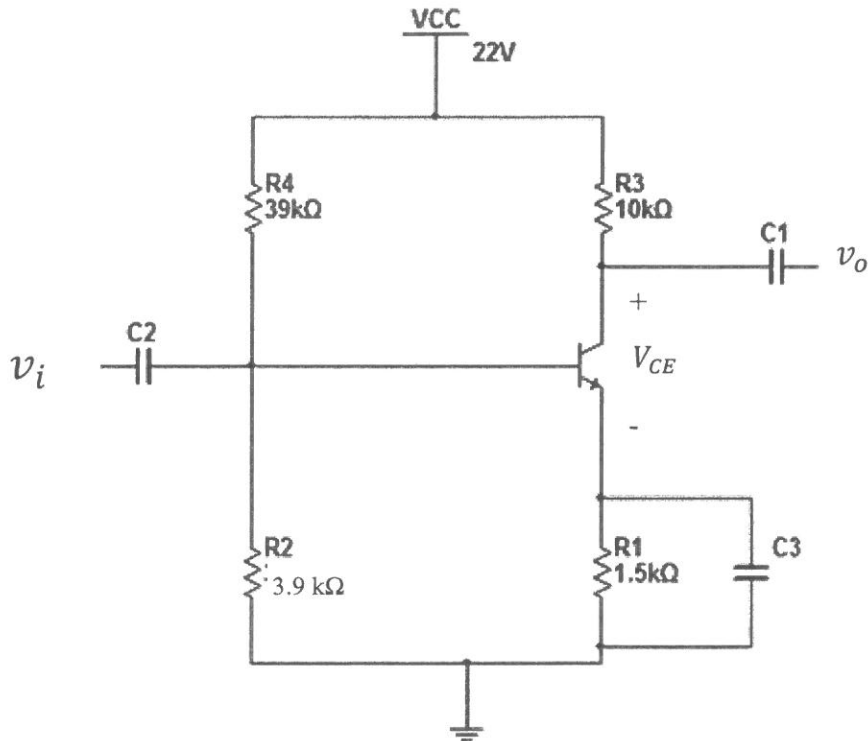


Figure 5(a)

- (a) Figure 5(a) shows the circuit diagram of a NPN transistor with $\beta=100$ and output impedance $r_o=50\text{k}\Omega$. v_i is the small signal input and v_o is the output. The capacitances of C1, C2 and C3 are assumed to be very large value.
- Determine the DC bias voltage V_{CE} , currents I_E , I_C and I_B using Exact Analysis. (12 marks)
 - Draw the r_e equivalent model of the circuit. (5 marks)
 - Determine the parameters of the system: input impedance Z_i , output impedance Z_o and gain A_v . (8 marks)

Question 6 (25 marks)

- (a) Refer to the circuit in Figure 6(a), the Bipolar Junction Transistor (BJT) is used as an inverter. Given that $I_{Csat} = 10 \text{ mA}$ and $\beta = h_{FE} = 250$, determine the values of R_B and R_C with explanation.

(13 marks)

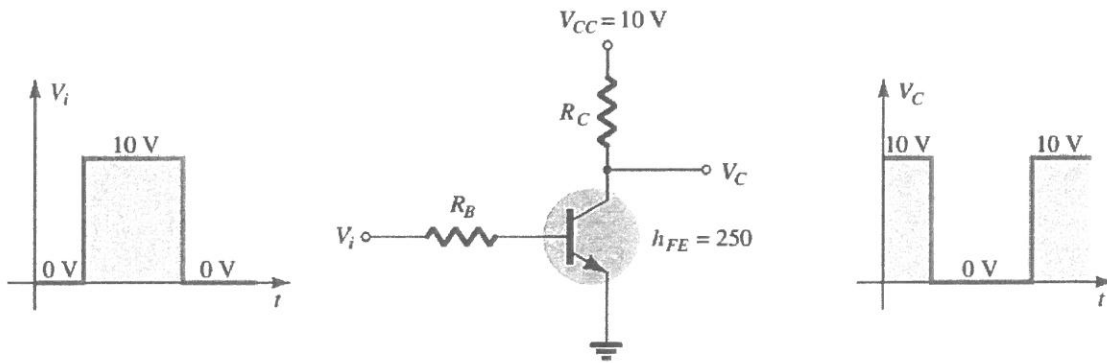


Figure 6(a)

(b) Figure 6(b) illustrates a fixed-biased configuration of field effect transistor (FET) circuit. Given that the Shockley's equation is $I_D = I_{DSS}(1 - \frac{V_{GS}}{V_P})^2$, using Mathematical Approach,

(i) find V_{GSQ} and I_{DQ} .

(4 marks)

(ii) calculate V_{DS} , V_D , V_G and V_S .

(8 marks)

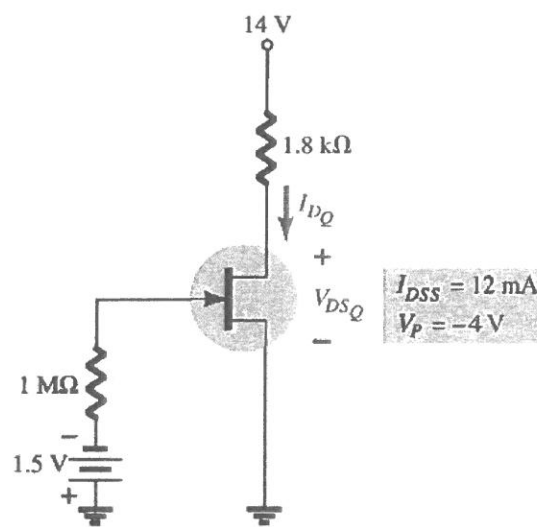


Figure 6(b)

- THE END -
 ALL THE BEST
 EEE1105 (AUG18)

