



INTI
International College Penang

FINAL
Examination Paper

(COVER PAGE)

Session : August 2019

Programme : Diploma in Electrical and Electronic Engineering (DEEI)

Course : EEE1105: Circuit Theory and Electronic Devices

Date of Examination : 9 December 2019 (Monday)

Time : 2:00pm – 4:00pm Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

IMPORTANT NOTE : THIS PAPER SHOULD NOT BE TAKEN OUT OF THE EXAMINATION HALL

Materials permitted : Non-Programmable Scientific Calculator

Materials provided : Appendix A (on page 8)

Examiner(s) : Mr. Chai Yoon Yik

Moderator : Prof. Ir. Dr. Mandeep Singh

This paper consists of 9 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)
 EEE1105: CIRCUIT THEORY AND ELECTRONIC DEVICES
 FINAL EXAMINATION: AUGUST 2019 SESSION

Instructions: This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Question 1

(a) For the network shown in Figure Q1(a), calculate:

- (i) The total resistance, R_T of the circuit. [3]
- (ii) The I_2 , I_6 , I_S , and V_5 . [8]
- (iii) The I_S again when there is a short circuit across R_1 . [1]

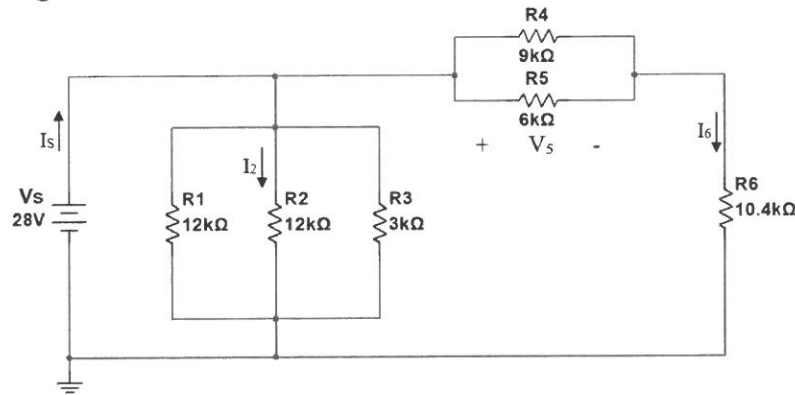


Figure Q1(a)

(b) A DC network is shown in Figure Q1(b). Calculate the value of the nodal voltage V_1 , V_2 and V_3 using Nodal analysis. [9]

 


Figure Q1(b)

- (c) Determine the potential difference V_1 in the Figure Q1(c). [4]

 


Figure Q1(c)

Question 2

- (a) A 230 V, 50 Hz AC power supply is connected to an inductive load with resistance of 8Ω and inductance of 0.05 H. Determine the:

- (i) Impedance of the load in polar form. [2]
- (ii) Magnitude and phase angle of the load current. [2]
- (iii) Apparent power and power factor. [4]
- (iv) Real power supplied to the load. [2]
- (v) Reactive power supplied to the load. [2]

- (b) A capacitor is connected in parallel to the load in (a) to increase the power factor to unity. Determine:

- (i) The required capacitance value. [4]
- (ii) The change in supply current from the uncorrected to the corrected power factor system. [2]

- (c) Explain the phenomenon of a series R-L-C resonant circuit using a frequency response plot. Why Q factor is very important parameter in a resonant circuit? [7]

Question 3

- (a) Determine the current I flows through R_1 resistor in. [6]

 


Figure Q3(a)

- (b) Given a network in Figure Q3(b), using the superposition principle, find:

 


Figure Q3(b)

- (i) The current through each resistor. [8]
 - (ii) The power dissipated in R1. [2]
- (c) Determine the Thévenin equivalent circuit for the network external to the resistor R_L in Figure Q3(c). [9]

 


Figure Q3(c)

Question 4

- (a) Briefly describe the following terms:
- (i) n-type silicon [1]
 - (ii) p-type silicon [1]
 - (iii) Donor impurity [1]
 - (iv) Acceptor impurity [1]
 - (v) Majority carrier [1]
 - (vi) Minority carrier [1]
- (b) Describe in your own words the conditions established by forward- and reverse-bias conditions in a p–n junction diode and how the resulting current is affected. [6]
- (c) Draw the V_o signal for the diode circuit with V_i as shown in the Figure Q4(c). All the important details must be indicated in the drawing. Appropriate calculation illustration also required in your answer. [8]

 
 


Figure Q4(c)

- (d) How do you transform the V_i into V_o signal as shown in Figure Q4(d) using a diode circuit?

 


Figure Q4(d)

[5]

Question 5

- (a) A BJT transistor 2N2222A is used in a signal amplifier circuit as shown in the Figure Q5(a).

 


Figure Q5(a)

Using the I-V characteristics shown in the Appendix A, do the followings:

- (i) Draw a load line on the characteristics determined by $E = 21\text{ V}$ and $R_L = 3\text{ k}\Omega$. Attach the Appendix A to your answer booklet. [2]
 - (ii) Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point. [2]
 - (iii) What are the resulting values of I_{CQ} and V_{CEQ} ? [1]
 - (iv) What is the value of β at the operating point? [1]
 - (v) What is the value of α defined by the operating point? [1]
 - (vi) What is the saturation current $I_{C\text{sat}}$ for the design? [1]
 - (vii) What is the dc power dissipated by the device at the operating point? [1]
 - (viii) What is the power supplied by dc supply E? [1]
 - (ix) What is the power loss of the amplifier? [1]
- (b) List the three different regions of a BJT transistor output characteristics. Explain an application for each region. [4]
- (c) For the emitter-bias network of Figure 5(c) with the $\beta = 50$, determine:
- (i) I_B and I_C [3]
 - (ii) V_{CE} [2]
 - (iii) V_C , V_E and V_B [3]
 - (iv) V_{BC} [2]

 


Figure Q5(c)

Question 6

(a) What are the major differences between the collector characteristics of a BJT transistor and the drain characteristics of a JFET transistor? [4]

(b) (i) Sketch the transfer characteristics directly from the drain characteristics given in Figure Q6(b). [4]

 


Figure Q6(b)

(ii) Using Figure Q6(b) to find the values of I_{DSS} and V_P , sketch the transfer characteristics using the Shockley's equation. [4]

(c) For the JFET network of Figure Q6(c), when the $V_D = 9V$, determine:

 


Figure Q6(c)

- | | | |
|-------|--------------------|-----|
| (i) | I_D | [2] |
| (ii) | V_S and V_{DS} | [3] |
| (iii) | V_G and V_{GS} | [2] |
| (iv) | V_P | [2] |

(d) Sketch all the four symbols for enhancement type MOSFET. [4]

-----End-----

Question: _____

Name: _____ Student No: _____

Appendix A

Transistor 2N2222A I_C vs V_{CE} curve

