



**FINAL
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : August 2021

Programme : Diploma in Electrical & Electronic Engineering (DEEI)

Course : EEE1105: Circuit Theory & Electronic Devices

Date of Examination : 4 December 2021 (Saturday)

Time : 8.00am – 11.00am Reading Time : Nil

Duration : 3 Hours

Special Instructions :

This paper consists of **FOUR (4)** questions. All the questions carry equal marks.

Material permitted : Non-Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Dr Su Hsio Wei

Chief Moderator : Chai Yoon Yik

This paper consists of 6 printed pages, including the cover page

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)
 EEE1105: CIRCUIT THEORY & ELECTRONIC DEVICES
 FINAL ALTERNATIVE ASSESSMENT: AUGUST 2021 SESSION

Instructions: This paper consists of **FOUR (4)** questions. All the questions carry equal marks.

Question 1 [25]

- (a) A two sources circuit is shown in Figure Q1(a). Using nodal analysis, calculate the node voltages V_1, V_2 and V_3 . [9]

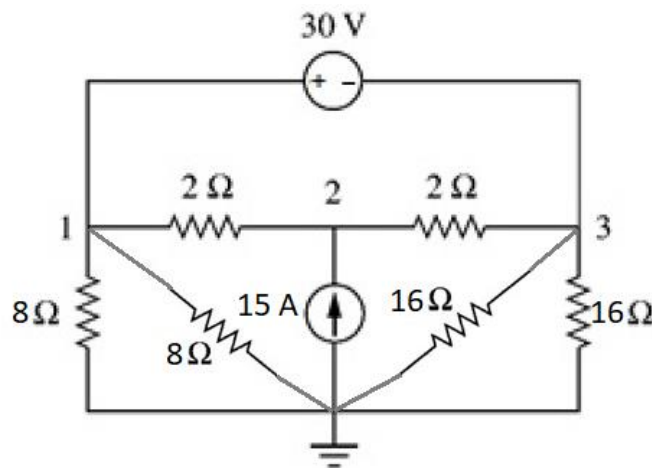


Figure Q1(a)

- (b) In the network of Figure Q1(b), using mesh analysis, calculate I_o and V_{ab} . [9]

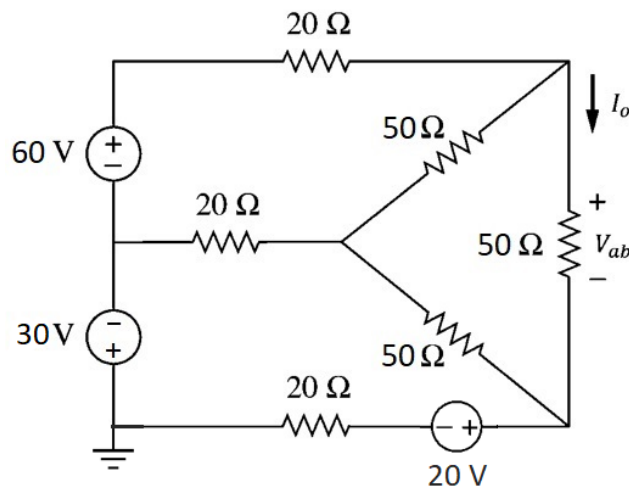


Figure Q1(b)

- (c) Using superposition principle, find the current I through E_2 for the network in Figure Q1(c). [7]

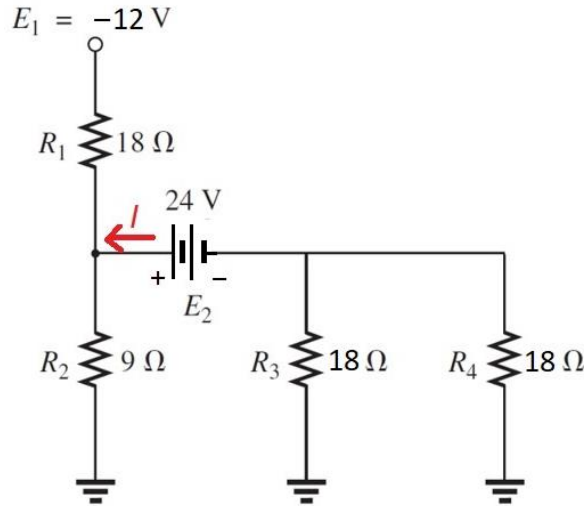


Figure Q1(c)

Question 2 [25]

- (a) Figure Q2(a) shows an electrical circuit with an alternating current source of $5 \angle 30^\circ$ A.

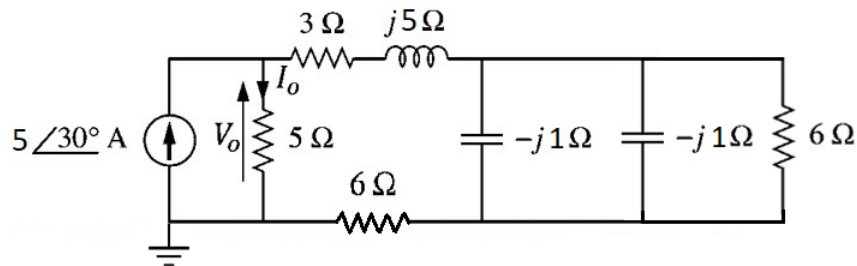


Figure Q2 (a)

Calculate:

- (i) The current phasor I_o and voltage phasor V_o . [4]
 - (ii) The complex power and the power factor of the circuit. [2]
 - (iii) The average power delivered by the source. [2]
 - (iv) The reactive power of the circuit. [2]
- (b) For the series RLC circuit in Figure Q2(b), find:

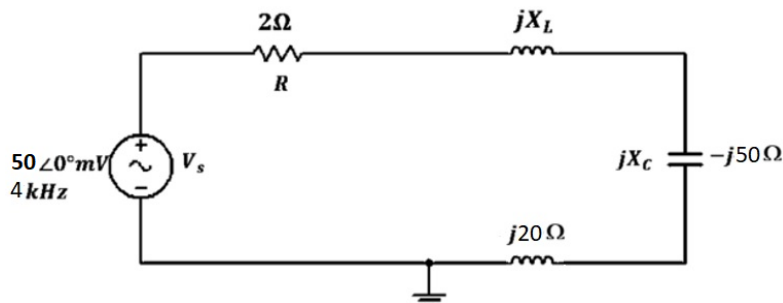


Figure Q2 (b)

- (i) The value of X_L for resonance. [1]
- (ii) The magnitude of the circuit current, I at resonance. [2]
- (iii) The voltage V_R, V_L and V_C at resonance. [3]
- (iv) The quality factor of the circuit. [1]
- (v) The value of total L and C at resonant frequency. [2]
- (vi) The bandwidth of the frequency response. [2]
- (vii) The low and high cutoff frequencies. [2]
- (viii) The power dissipation at -3dB frequency. [2]

Question 3 [25]

(a) Figure Q3(a) shows an RC circuit with the switch is opened at $t = 0$.

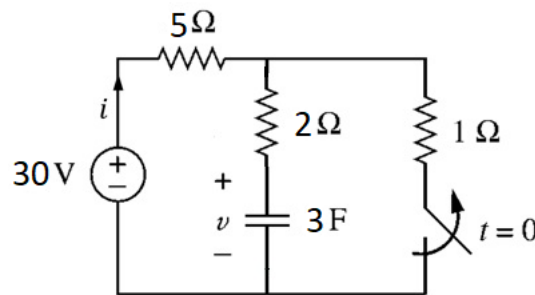


Figure Q3(a)

- (i) Determine the $v(t)$ and $i(t)$ at $t = 0$. [2]
 - (ii) Determine the $v(t)$ and $i(t)$ for $t > 0$. [7]
 - (iii) Sketch the $v(t)$ and $i(t)$ for (i) and (ii). [4]
 - (iv) Determine the energy stored in the capacitor at steady-state. [2]
- (b) Explain how to produce n-type and p-type silicon. List down their important properties. [4]
- (c) For the network of Figure Q3(c), determine the maximum of V_i that will maintain V_L at 7.6V and not exceed the maximum power rating of the Zener diode. [6]

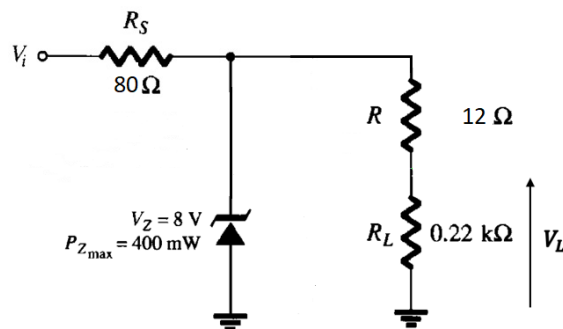


Figure Q3(c)

Question 4 [25]

(a) A bipolar junction transistor is connected in voltage-divider-bias configuration as shown in the Figure Q4(a).

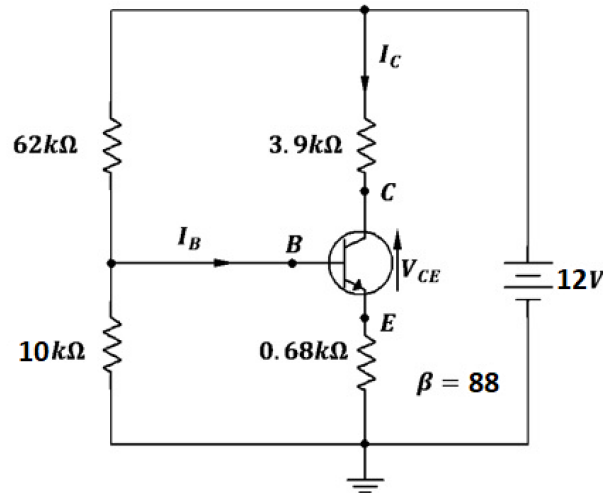


Figure Q4(a)

Using exact approach analysis, calculate:

- | | | |
|-------|-------------------------------------|-----|
| (i) | I_{BQ} | [4] |
| (ii) | I_{CQ} | [1] |
| (iii) | V_{CEQ} | [2] |
| (iv) | V_{CQ} | [2] |
| (v) | V_{EQ} | [2] |
| (vi) | V_{BQ} | [2] |
| (vii) | <i>transistor power dissipation</i> | [2] |

(b) Figure Q4(b) shows an n-enhancement mode P-MOSFET circuit.

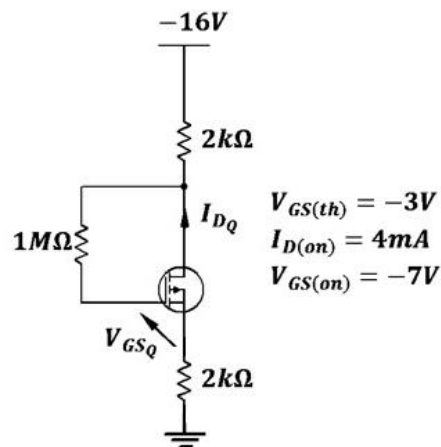


Figure Q4(b)

- (i) Draw the transfer characteristics and bias line of the circuit. [5]
- (ii) Calculate the V_{GSQ} and I_{DQ} . [2]
- (iii) Calculate the V_D . [2]
- (iv) State the region of the drain characteristic the MOSFET operates in. [1]

~THE END~

EEE1105 (F)/ August 2021 Session/ formatted