



**FINAL
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : August 2021

Programme : Diploma in Electrical & Electronic Engineering (DEEI)

Course : EEE2112: Introduction to Power Electronics & Drives

Date of Examination : 5 December 2021 (Sunday)

Time : 2.00pm – 5.00pm Reading Time : Nil

Duration : 3 Hours

Special Instructions :

This paper consists of **FOUR (4)** questions. Answer all **FOUR (4)** questions. All questions carry equal marks.

Material permitted : Non-Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Alan Wong Kam Mun

Chief Moderator : Richard Lai

This paper consists of 4 printed pages, including the cover page

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)

EEE2112: INTRODUCTION TO POWER ELECTRONICS AND DRIVERS

FINAL ALTERNATIVE ASSESSMENT: AUGUST 2021 SESSION

Instructions: This paper consists of **FOUR (4)** questions. Answer all **FOUR (4)** questions. All questions carry equal marks.

Important notice: Computer software are **NOT** allowed in this exam except software to access the Question Paper and to submit the Answer Script. Answers are expected to be hand-written and required graph are to be manually plotted. Copy/paste and computer plotted graph will get zero marks.

Question 1

- a. A single-phase 110 V, 500 W load is connected to single-phase 110 V, 50 Hz supply through a SCR as shown in Figure Q1(a). Find the RMS power delivered to the load for a SCR firing angle delays of 45° . [15]

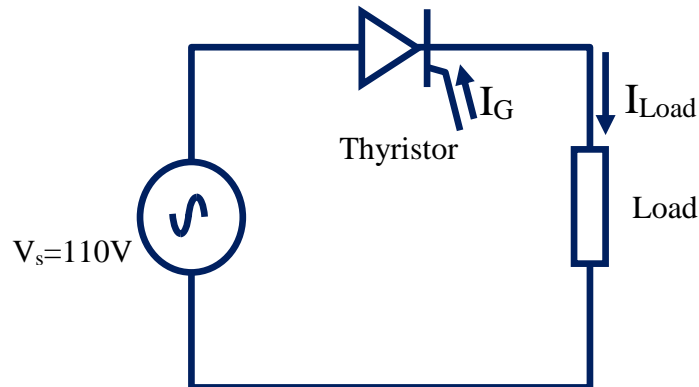


Figure Q1(a)

b. A single-phase bridge controlled rectifier as shown in Figure Q1(b), fed with single phase 230 V 50 Hz ac supply is used to control the dc supply. Assume the load consists of resistance $R_L = 10 \Omega$ and L is very large (infinite).

(i) Find the average output voltage given that the firing angle of the SCR is 30° and 210° .

[6]

(ii) Sketch the load voltage if freewheeling diode connected across the load.

[4]

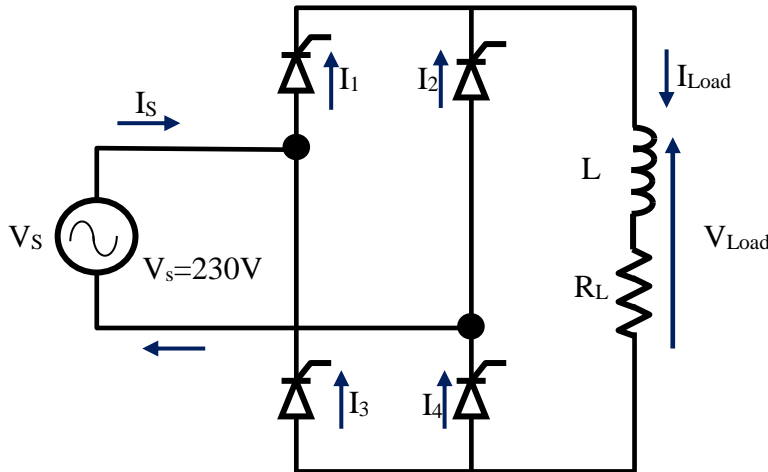


Figure Q1(b)

Question 2

A dc step-down converter connect to 48 V battery produces an output voltage of 18 V across a 10Ω resistive load with output voltage ripple less than 0.5 percent. Assume ideal components characteristic with the inductance 25% larger than the minimum value and switching frequency is 40 kHz, find:

(i) The duty ratio. [2]

(ii) The value of the inductor. [4]

(iii) The value of the capacitor. [4]

(iv) The peak current and peak voltage at the inductor and capacitor respectively.

[5]

(v) The rms current rating for the inductor. [3]

(vi) The voltage and current rating of the capacitor and inductor respectively. Assume 100% safely margin. [4]

(vii) The voltage and current rating of the switching device. Assume 100% safely margin. [3]

Question 3

A single phase full-bridge inverter has a resistive load of $R= 3 \Omega$ and the DC input voltage $V_{dc}= 24 \text{ V}$. The switching elements used are power MOSFET. Find :

- The total harmonic distortion THD. [3]
- The distortion factor DF. [8]
- The harmonic factor and distortion factor of the 3rd harmonic only. [5]
- The real output power at the resistive load. [2]
- The peak current at the load. [2]
- The average current at each switching element. [2]
- The switching frequency for each switching element is 100 Hz, what is the frequency of the square wave generated. [1]
- The new output power at the resistive load when an ideal 100 Hz low pass filter is connected to the inverter output. [2]

Question 4

A single phase full-wave AC chopper is shown in Figure Q4 below has a resistive load $R = 10 \Omega$ and the input voltage is $V_s = 120 \text{ V}_{rms}$, 50 Hz. The firing angles of thyristor T1 and T2 are equal: $\alpha_1 = \alpha_2 = 90^\circ$.

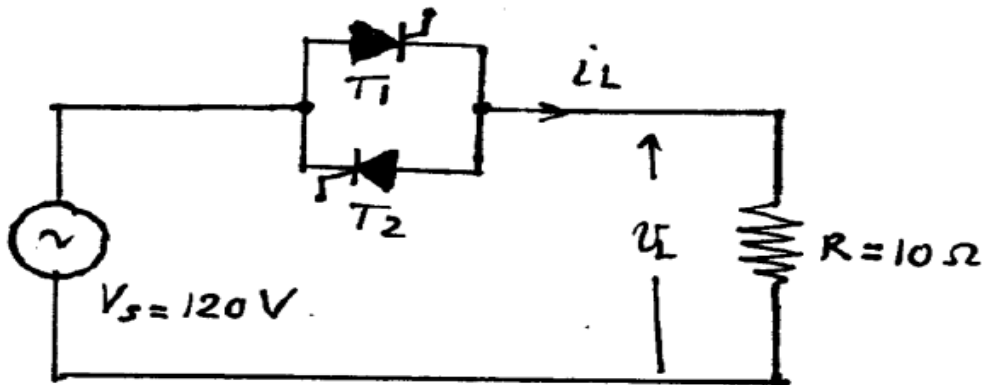


Figure Q4

- Sketch (draw and label) the output waveform at V_L . [5]
 - Find the rms output voltage V_{Lrms} . [4]
- Find the input power factor. [8]
- Find the average and rms values of the thyristor current. [8]

~THE END~