



**FINAL  
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : August 2020

Programme : Diploma in Electrical & Electronic Engineering (DEEI)

Course : EEE1105: Circuit Theory & Electronic Devices

Date of Examination : 14 December 2020 (Monday)

Time : 8.00am – 11.00am Reading Time : Nil

Duration : 3 Hours

**Special Instructions :**

This paper consists of **FOUR (4)** questions. Answer all the questions. All questions carry equal marks.

**Answer script Blackboard submission requirement:**

- Submit your softcopy answer script **ONE** time only to Blackboard.
- Write on top of each page of the answer script student Inti ID or name, subject code and page number. *Example: P20209539 / EEE1105 / Page 2 of 5.*
- Arrange your answer in proper order, scan the answer scripts and submit it to Blackboard within the given examination allocated time. Late submission is **NOT** allowed.
- Use a proper scanner or CamScanner on your mobile for scanning. Combine all pages in **ONE PDF file** for submission to Blackboard. Filename: **EEE1105 Final Exam (Name).PDF**
- Make sure pages of answer script are scanned with the good contrast and readable quality.
- Marking will be based on the scanned document as final.

Material permitted : Non-Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Chai Yoon Yik

Chief Moderator : Steven Khoo Boo Tap

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)  
 EEE1105: CIRCUIT THEORY & ELECTRONIC DEVICES  
 FINAL ALTERNATIVE ASSESSMENT: AUGUST 2020 SESSION

Instructions: This paper consists of **FOUR (4)** questions. Answer all the questions. All questions carry equal marks.

**Question 1 [25]**

- (a) A multiple sources network is shown in Figure Q1(a). Using nodal analysis, calculate the current passing through each resistor. [10]

 


Figure Q1(a)

- (b) In the circuit of Figure Q1(b), using mesh analysis, calculate  $i_1$ ,  $i_2$ , and  $i_3$ . [9]

 


Figure Q1(b)

- (c) Find the Norton equivalent ( $I_N$ ,  $R_N$ ) with respect to terminals a-b in the circuit as shown in Figure Q1(c). [6]

 


Figure Q1(c)

**Question 2 [25]**

- (a) Figure Q2(a) shows an electrical circuit connection with sinusoidal voltage source of 50Hz.

 


Figure Q2 (a)

Calculate:

- (i) The complex power and the power factor of the circuit. [4]
  - (ii) The average power delivered by the source. [2]
  - (iii) The reactive power of the circuit. [2]
  - (iv) The apparent power of the circuit. [2]
- (b) Suggest how to increase the power factor of the circuit to unity without affecting the total average power delivered by the source? Your solution must have relevant calculation and justification. [6]

- (c) Consider the phase shifting circuit in Figure Q2(c). Let the  $v_i = 120\angle 0^\circ V$  operating at 60Hz.

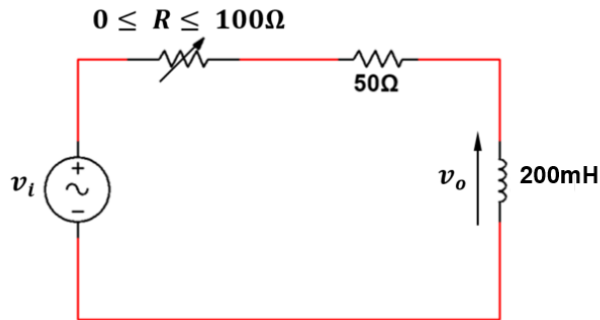


Figure Q2(c)

Calculate:

- (i) The  $v_o$  when R is maximum. [3]
- (ii) The  $v_o$  when R is minimum. [2]
- (iii) The R that will produce a current with phase shift of  $45^\circ$ . [4]

**Question 3 [25]**

- (a) Figure Q3(a) shows an electronic flash lamp which has a charging current-limiting resistor of  $6k\Omega$  and a  $2mF$  electrolytic capacitor. Assume the capacitor is charged to 240 V and the lamp resistance is  $12\Omega$ , calculate:

 


Figure Q3(a)

- (i) The peak charging current. [2]
- (ii) The time required for the capacitor to be fully charged. [2]
- (iii) The peak discharging current. [2]
- (iv) The total energy stored in the capacitor. [2]
- (v) The average power dissipated by the lamp. [2]

- (b) Explain why there is a 0.7V developed across a forward-bias silicon pn junction. [5]
- (c) Design a diode circuit to perform the function indicated in Figure Q3(c). Assume an ideal diode. Explain the circuit operation. [10]

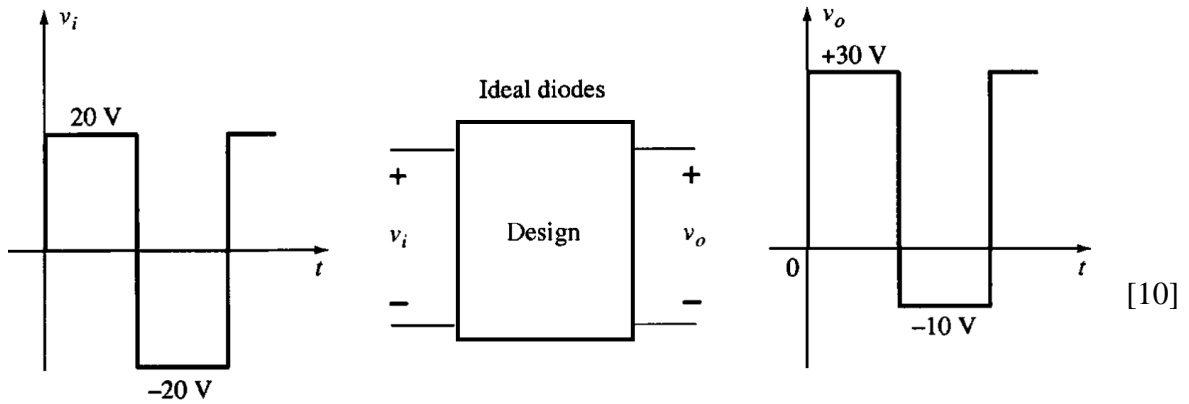


Figure Q3(c)

**Question 4 [25]**

- (a) A bipolar junction transistor is connected in emitter-bias configuration as shown in the Figure Q4(a). If the Q-point is defined at  $I_{CQ} = 4mA$  and  $V_{CEQ} = 10V$ , calculate:

 


Figure Q4(a)

- (i)  $R_C$  [4]
- (ii)  $\beta$  at Q-point. [2]
- (iii)  $R_B$  [2]
- (iv)  $V_E$  [2]
- (v) *transistor power dissipation* [2]

(b) Sketch the channel condition in an n-channel enhancement-type MOSFET structure for each of the following conditions:

- $V_{GS} = 0$
- $V_{GS} > 0$  and  $V_{DS} = 0$
- $V_{GS} > 0$  and  $V_{DS} > 0$

[3]

(c) Figure Q4(c) shows an n-depletion mode MOSFET circuit.

 


Figure Q4(c)

- |       |  |     |
|-------|--|-----|
| (i)   | Draw the transfer characteristics and bias line of the circuit.  | [4] |
| (ii)  | Determine the $V_{GSQ}$ and the $I_{DQ}$ from (i).               | [2] |
| (iii) | Calculate the $V_{DSQ}$ and the $V_S$ .                          | [3] |
| (iv)  | Which region of the drain characteristic the MOSFET operates in? | [1] |

~THE END~