



**FINAL
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : April 2021

Programme : Diploma in Electrical & Electronic Engineering (DEEI)

Course : EEE2101: Introduction to Digital Electronics

Date of Examination : 28 July 2021 (Wednesday)

Time : 2.00pm – 5.00pm Reading Time : Nil

Duration : 3 Hours

Special Instructions :

This paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry equal marks.

Material permitted : Non-Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Steven Khoo Boo Tap

Chief Moderator : Chan Tse Wei

*This paper consists of **10** printed pages, including the cover page*


INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)
 EEE2101: INTRODUCTION TO DIGITAL ELECTRONICS
 FINAL ALTERNATIVE ASSESSMENT: APRIL 2021 SESSION

Instructions: This paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry equal marks.

Question 1

 - (a) Present the following Boolean expressions according to the stated simplest form, using the specified method:
- (i) $F_1(W, X, Y, Z) = \sum m(0,5,10,15) + d(2,7,8,13)$
 Simplest Form: Any type of gate implementation deemed appropriate.
 Method: Karnaugh Map and/or Boolean Algebra. (4 marks)
- (ii) $F_2(R, S, T, U) = \prod M(1,2,4,7,8,11,13,14) \cdot \prod d(3,6,9,12)$
 Simplest Form: Any type of gate implementation deemed appropriate.
 Method: Karnaugh Map and/or Boolean Algebra. (4 marks)
- (iii) $F_3(K, L, M, N) = \sum m(0,1,2,4,6,8,10,11,12,14) + d(3,9)$
 Simplest Form: Any type of gate implementation deemed appropriate.
 Method: Karnaugh Map and/or Boolean Algebra. (4 marks)
- (b) (i) Produce the simplest Boolean expression for F in Figure 1(b) and present the minimum expression using Boolean simplification method only. (6 marks)
- (ii) Suggest only one type of gate to represent the simplified expression and state the IC part number for the implementation. (2 marks)
- Show all workings clearly.



- (b) A NOR SR latch is driven by a 2-bit binary counter with outputs designated B_1B_0 (B_1 is the MSB) through a combinational logic circuit. Output B_1 is ANDed with $(B_1 \oplus B_0)$ and drives the R input of the SR latch. B_0 is also ANDed with $(B_1 \oplus B_0)$ and drives the S input.
- (i) Draw the logic circuit showing the signals, B_1 & B_0 and output, Q of the SR latch. (2.5 marks)
- (ii) Construct a table to record the output, Q of the SR latch as the counter steps through its 4 states beginning with $B_1B_0 = 00$. Assume the output is initially RESET. (2.5 marks)
- (c) Figure 2(c) shows a 4-bit synchronous counter, which is designed to perform a specific counting sequence.

Flip-flop FF3 is MSB and flip-flop FF0 is LSB. Flip-flop J_3K_3 has output Q_3 , flip-flop J_2K_2 has output Q_2 , flip-flop J_1K_1 has output Q_1 and flip-flop J_0K_0 has output Q_0 . Assume all flip-flops are initially in 0000 (State 0) for $Q_3Q_2Q_1Q_0$ outputs.

 


Figure 2(c)

Show all workings clearly according to the procedures listed in part (c)(i), (c)(ii), (c)(iii) and (c)(iv).

- (i) Provide the excitation expressions for each of the flip-flops in Figure 2(c). (4 marks)
- (ii) Produce the Karnaugh maps according to the excitation expressions obtained in part (c)(i). (4 marks)
- (iii) Build the transition table/next state table from the Karnaugh maps obtained in part (c)(ii). (5 marks)
- (iv) Sketch the state diagram and comment on the states obtained. (2 marks)

Question 3

- (a) Solve the numbering system transformation of $[156.32_8 \times 10.625_{10}]$ to its binary equivalent with 8 binary points accuracy. Show all workings clearly. (5 marks)
- (b) Table 3(b) shows a portion of a quadruple 2-input XOR gates (DM7486) datasheet. Compute the following parameters from this datasheet, show all workings clearly:
 - (i) Power dissipation, $P_{D(max)}$ on a DM7486 IC when the output condition is as shown in Figure 3(b). Assume that the V_{CC} used is maximum. (4 marks)

 


Figure 3(b)

- (ii) Fan-out, the number of gates from the same IC family that can be safely driven by an output under worst-case consideration. (3 marks)
- (iii) Noise Margin voltages, V_{NL} and V_{NH} . (3 marks)

Table 3(b)

Recommended Operating Conditions

Symbol	Parameter	Min	Nom	Max	Units
V_{CC}	Supply Voltage	4.75	5	5.25	V
V_{IH}	HIGH Level Input Voltage	2			V
V_{IL}	LOW Level Input Voltage			0.8	V
I_{OH}	HIGH Level Output Current			-0.4	mA
I_{OL}	LOW Level Output Current			8	mA
T_A	Free Air Operating Temperature	0		70	°C

Electrical Characteristics

over recommended operating free air temperature range (unless otherwise noted)

Symbol	Parameter	Conditions	Min	Typ (Note 2)	Max	Units
V_I	Input Clamp Voltage	$V_{CC} = \text{Min}, I_I = -18 \text{ mA}$			-1.5	V
V_{OH}	HIGH Level Output Voltage	$V_{CC} = \text{Min}, I_{OH} = \text{Max},$ $V_{IL} = \text{Max}, V_{IH} = \text{Min}$	2.7	3.4		V
V_{OL}	LOW Level Output Voltage	$V_{CC} = \text{Min}, I_{OL} = \text{Max},$ $V_{IL} = \text{Max}, V_{IH} = \text{Min}$		0.35	0.5	V
		$I_{OL} = 4 \text{ mA}, V_{CC} = \text{Min}$		0.25	0.4	
I_I	Input Current @ Max Input Voltage	$V_{CC} = \text{Max}, V_I = 7V$			0.2	mA
I_{IH}	HIGH Level Input Current	$V_{CC} = \text{Max}, V_I = 2.7V$			40	μA
I_{IL}	LOW Level Input Current	$V_{CC} = \text{Max}, V_I = 0.4V$			-0.6	mA
I_{OS}	Short Circuit Output Current	$V_{CC} = \text{Max}$ (Note 3)	-20		-100	mA
I_{CCH}	Supply Current with Outputs HIGH	$V_{CC} = \text{Max}$ (Note 4)		6.1	10	mA
I_{CCL}	Supply Current with Outputs LOW	$V_{CC} = \text{Max}$ (Note 5)		9	15	mA

Note 2: All typicals are at $V_{CC} = 5V, T_A = 25^\circ\text{C}$.

Note 3: Not more than one output should be shorted at a time, and the duration should not exceed one second.

Note 4: I_{CCH} is measured with all outputs OPEN, one input at each gate at 4.5V, and the other inputs grounded.

Note 5: I_{CCL} is measured with all outputs OPEN and all inputs grounded.

Switching Characteristics

at $V_{CC} = 5V$ and $T_A = 25^\circ\text{C}$

Symbol	Parameter	Conditions	$R_L = 2 \text{ k}\Omega$				Units
			$C_L = 15 \text{ pF}$		$C_L = 50 \text{ pF}$		
			Min	Max	Min	Max	
t_{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	Other Input Low		18		23	ns
t_{PHL}	Propagation Delay Time HIGH-to-LOW Level Output			17		21	
t_{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	Other Input High		10		15	ns
t_{PHL}	Propagation Delay Time HIGH-to-LOW Level Output			12		15	

(c) The logic circuit in Figure 3(c) has three inputs (A, B, C) and two outputs (Y, Z).

 


Figure 3(c)

Table 3c(i) shows a portion of a quadruple 2-input AND gates datasheet.
 Table 3c(ii) shows a portion of a quadruple 2-input OR gates datasheet.
 Table 3c(iii) shows a portion of a quadruple 2-input XOR gates datasheet.
 Table 3c(iv) shows a portion of a hextuple NOT gates datasheet.

Table 3c(i)

Symbol	Parameter	Conditions	Min	Max	Units
t _{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	C _L = 15 pF R _L = 400Ω		27	ns
t _{PHL}	Propagation Delay Time HIGH-to-LOW Level Output			19	ns

Table 3c(ii)

Symbol	Parameter	R _L = 2 kΩ				Units
		C _L = 15 pF		C _L = 50 pF		
		Min	Max	Min	Max	
t _{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	3	11	4	15	ns
t _{PHL}	Propagation Delay Time HIGH-to-LOW Level Output	3	11	4	15	ns

Table 3c(iii)

Symbol	Parameter	Conditions	C _L = 15 pF, R _L = 400Ω		Units
			Min	Max	
t _{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	Other input LOW		23	ns
t _{PHL}	Propagation Delay Time HIGH-to-LOW Level Output			17	ns
t _{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	Other input HIGH		30	ns
t _{PHL}	Propagation Delay Time HIGH-to-LOW Level Output			22	ns

Table 3c(iv)

Symbol	Parameter	$R_L = 2\text{ k}\Omega$				Units
		$C_L = 15\text{ pF}$		$C_L = 50\text{ pF}$		
		Min	Max	Min	Max	
t_{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	3	10	4	15	ns
t_{PHL}	Propagation Delay Time HIGH-to-LOW Level Output	3	10	4	15	ns

- (i) Using the datasheets given, determine the maximum propagation delay time by considering all possible paths of Figure 3(c). Show all workings clearly. (8 marks)
- (ii) Determine the maximum operating frequency that can be applied to Figure 3(c) without affecting its functionality. Show all workings clearly. (2 marks)

Question 4

- (a) Compute the 2's complement number of -216.8125_{10} in signed binary numbering system. Assuming the binary system is a 10-bit system with 8 binary points. Show all workings clearly. (5 marks)
- (b) Figure 4(b) shows a computer controlling the speed of a motor. The 0 to 2mA analog current from the DAC is amplified to produce motor speeds from 0 to 1000 revolutions per minute (rpm).

 


Figure 4(b)

- (i) Compute the number of bits should be used if the computer is able to produce a motor speed that is within 4 rpm of the desired speed. (5 marks)
- (ii) Using the number of bits obtained in part (b)(i), compute the nearest motor speed (in rpm) achievable if 360 rpm is required. (5 marks)
- (c) Analog to Digital Converter (ADC) is an important element in signal processing for digital conversion of sensor signal. In a process to digitize a vibrating signal, an accelerometer (acceleration transducer) with the characteristics shown in Table 4(c) is used.

Table 4(c)

Sensitivity	(±5.0%) 25 mV/g
Measurement Range	±75 g peak
Frequency Range	(±5%) 10 to 15000 Hz
Sensing Element	Quartz
Weight	99 gram

Acceleration is quantified in terms of standard gravity (g). Assume the formula given is $resolution = \frac{V_{range}}{2^n - 1}$.

Apply an appropriate ADC for this sensor application by computing the:

- (i) Number of bits. (7 marks)
- (ii) Resolution. (3 marks)

~THE END~