



INTI

INTERNATIONAL COLLEGE PENANG (507232-U)
LAUREATE INTERNATIONAL UNIVERSITIES

INTI LIBRARY
INTI INTERNATIONAL COLLEGE PENANG

FINAL
Examination Paper

(COVER PAGE)

Session : JANUARY 2012

Programme : DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING

Course : EEE2101: INTRODUCTION TO DIGITAL ELECTRONICS.

Date of Examination : 5 March 2012

Time : 11a.m. – 1p.m. Reading Time : Nil

Duration : 2 Hours

Special Instructions :

This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

Materials permitted :

NON PROGRAMMABLE CALCULATOR

Materials provided : NIL

Examiner(s) : V.MEENAKSHI SUNDARAM

Moderator : KHOO BOO TAP

This paper consists of 5 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONICS ENGINEERING (DEE)

EEE 2101: INTRODUCTION TO DIGITAL ELECTRONICS
FINAL EXAMINATION: JANUARY 2012 SESSION

Instructions: This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

Question 1

- (a) (i) Subtract 33_H from $B8_H$, express the answer in binary number. (2 marks)
- (ii) Determine the decimal value of given signed binary number expressed in sign magnitude: 10010101. (3 marks)
- (iii) Convert 0.12_{10} to hexadecimal number. (3 marks)
- (b) Convert the decimal number 0.3112_{10} into binary number. (3 marks)
- (c) Perform the following subtraction of the signed binary numbers using 2's complement method:
 $0000\ 1000_2 - 00000011_2$ (4 marks)
- (d) (i) Inputs A and B are applied to a NOR gate. Inputs B and C are applied to a second NOR gate. The outputs of the two NOR gates are then applied to a NAND gate. Determine the Boolean equation of the output F of the circuit. (4 marks)
- (ii) Use De Morgan's rules to prove that a coincidence gate provides the inverse function to an exclusive OR gate. (6 marks)

Question 2

- (a) Using Boolean Algebra simplify the following Boolean expression:
 $F = \overline{AB} + \overline{AC} + \overline{ABC}$. (4 marks)
- (b) (i) Design the logic circuit for the following equation by using NOR gates only.
 $F = \overline{AB} + \overline{AB}$. (4 marks)
- (ii) Inputs A and B are applied to the inputs of a 2-input NAND gate. Inputs C and B are applied to the inputs of another 2-input NAND gate. The outputs of the two NAND gates are applied to a NOR gate. Show that the circuit could be replaced by one 3-input AND gate. (6 marks)
- (c) (i) Draw and explain the half adder circuit. (4 marks)
- (ii) Define Demultiplexers. (3 marks)
- (iii) Prove that $A + \overline{AB} = A + B$ (4 marks)

Question 3

- (a) (i) Convert the following SOP expression to an equivalent POS expression
 $\overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC}$. (4 marks)
- (ii) Reduce to its simplest form
 $F = \overline{(A + \overline{B} + C)} + \overline{(A + \overline{B} + C + D)} + \overline{(A + B + \overline{C} + D)} + \overline{(A + C)}$ (6 marks)
- (iii) Use a K-map to minimize the following SOP expression:
 $\overline{BCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD}$. (4 marks)
- (b) Draw the logic circuit diagram for the following expression
(i) $AB + A(B+C) + B(B+C)$ (3marks)
(ii) $B+AC$ also prove that these two equations are equivalent. (2marks)
- (c) Design the logic circuit for the following equation by using NOR gates only.
 $F = \overline{AB} + \overline{AB}$. (6 marks)

Question 4

- (a) Define
- (i) Word capacity expansion. (3 marks)
 - (ii) Word length expansion. (3 marks)
- (b) Design a decoder using the 16×8 PROM which accepts BCD inputs 0000 through 1001, and displays the letter A through J, respectively on a common cathode 7-segment display. (15 marks)
- (c) Define PROM. (4 marks)

Question 5

- (a) (i) How many conditional flags associated with the 8085 microprocessor? Explain them with examples. (5 marks)
- (ii) Write a program to subtract 04_H in the B register from 08_H in the C register and store the result in a memory location of 8150_H . The program should halt at the end of execution. (6 marks)
- (b) With the aid of a diagram describe Ramp type analog to digital conversion. (8 marks)
- (c) A weighted resistor DAC has $R_f = 20K\Omega$ and $R = 12.5K\Omega$. Calculate its output voltage when the 4-bit digital input word is (i) 1010, and (ii) 0101. Logic 1 voltage = 5V. (6 marks)

Question 6

- (a) (i) A weighted resistor type 4-bit DAC uses a voltage of 5 V and the feedback resistor is 1000Ω . If the output voltage produced by the LSB is to be 0.05 V, determine the required value for R. (4 marks)
- (ii) Draw the logic symbol and truth table for X-NOR gate. (4 marks)
- (b) (i) An 8-bit DAC of the binary weighted type uses a lowest resistor value of $1k\Omega$. Calculate the values required for the other resistors. Comment on your answer. (4 marks)
- (ii) Calculate the resolution of a 12 bit ADC and find equivalent value for a 10 V input voltage range. (5marks)
- (c) Explain the operation and write the addressing method and flags involved in the following instructions
- (i) LDA addr (2marks)
- (ii) MOV M,R (2marks)
- (iii) STA addr (2marks)
- (iv) MVI M, 04. (2marks)

--THE END--

EEE2101/ (F) JAN 2012/V. Meenakshi Sundaram