

INTI
International College Penang
LAUREATE INTERNATIONAL UNIVERSITIES®

FINAL
Examination Paper
(COVER PAGE)

Session : JANUARY 2015

Programmes : **DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING (DEED)**

Course : **EEE1105: CIRCUIT THEORY & ELECTRONIC DEVICES**

Date of Examination : 9 March 2015 (Monday)

Time : 11:00am – 1:00pm Reading Time: Nil

Duration : 2 Hours

Special Instructions :

This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

Students are not allowed to remove this question paper from the examination venue.

Materials permitted : Non Programmable Scientific Calculator

Materials provided: Graph paper with diode characteristic (for Question 3(C))

Examiner(s) : Ms. Shalyn Lim Sheue Hui

Moderator : Dr. Cheah Kean Seng

This paper consists of 12 printed pages, including the cover page.

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)

EEE 1105: CIRCUIT THEORY & ELECTRONIC DEVICES
FINAL EXAMINATION: JAN 2015 SESSION

Instructions: This paper consists of SIX (6) questions. Answer any FOUR (4) questions in the answer booklet provided. All questions carry equal marks.

Question 1

(a) With reference to Figure Q1(a).

(i) Calculate the currents I_1 , I_2 , and I_3 .

(3 marks)

(ii) Determine the values of the unknown resistors R_2 and R_3 .

(3 marks)

 


Figure Q1(a)

(b) Refer to Figure Q1(b), using nodal analysis calculate

(i) V_1 and V_2 .

(5 marks)

(ii) I_1 and I_4 .

(3 marks)

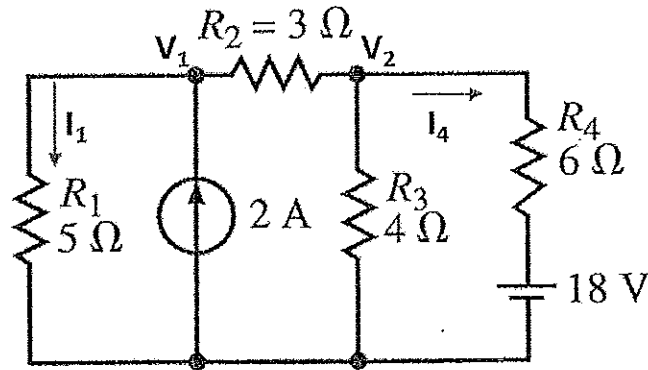


Figure Q1(b)

(c) For the circuit shown in Figure Q1(c), calculate

(i) Thevenin resistance R_{Th} .

(2 marks)

(ii) open terminal voltage V_{Th} using Thevenin's theorem.

(3 marks)

(iii) short circuit current I_N using Northan's theorem

(4 marks)

(iv) the maximum power transfer to the load, R across terminal a and b.

(2 marks)

 


Figure Q1(c)

Question 2

- (a) Voltage and current are out of phase by 40° , and voltage lags. Using current as the reference, sketch the phasor diagram and the corresponding waveforms. (3 marks)
- (b) For the network of Figure Q2(b), calculate [* answer in polar form]
- (i) the total impedance Z_T . (3 marks)
 - (ii) the voltage V_2 and the current I_L . (6 marks)
 - (iii) the power factor of the network. (2 marks)
 - (iv) the active and reactive power of the network. (3 marks)

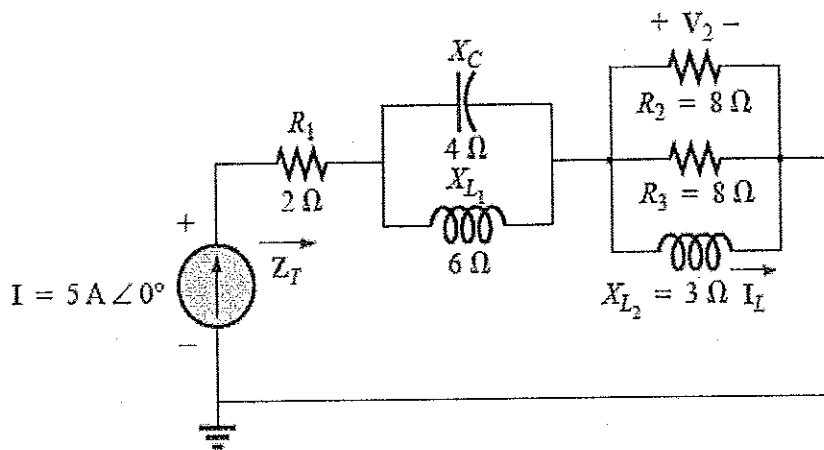


Figure Q2(b)

(c) Refer to the resonant network in Figure Q2(c),

- (i) Find the value of L if the resonant frequency is 1800 Hz. (2 marks)
- (ii) Find the magnitude of the current I_{rms} at resonance. (3 marks)
- (iii) Find the Q factor of the network. (3 marks)

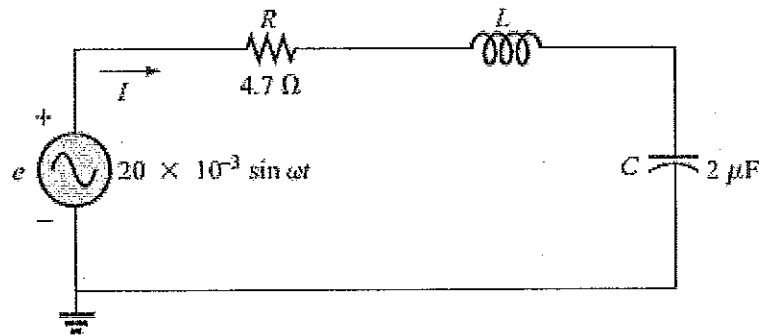


Figure Q2(c)

Question 3

(a) Sketch and label the output waveform for the clamper circuit shown in Figure Q3(a). Assume ideal diode and $RC \gg \frac{T}{2}$.

(3 marks)

 


Figure Q3(a)

(b) Refer to the half wave rectifier circuit shown in Figure Q3(b),

- (i) sketch the output waveform across R_L with proper labeling. (2 marks)
- (ii) calculate the average output voltage. (4 marks)
- (iii) what minimum PIV rating must the diodes have? (2 marks)

 


Figure Q3(b)

(c) For the series diode configuration of Figure Q3(c) (i) and the characteristic in Figure Q3(c) (ii), determine

- (i) V_{DQ} and I_{DQ} using the given graph paper with diode characteristic (**please attach with the answer script**). (7 marks)
- (ii) V_R (2 marks)

 


Figure Q3(c) (i)

 


Figure Q3(c) (ii)

- (d) Determine the power dissipation of the resistors and zener diode in Figure Q3(d). Given $V_S = 15V$, $R_S = 560\Omega$, $R_L = 2k\Omega$, $V_Z = 10V$. Assume the zener diode is ideal. Also, calculate the total power delivered by V_S .

(6 marks)

 


Figure Q3(d)

Question 4

- (a) Briefly describe how to operate BJT as an amplifier. (3 marks)
- (b) The biasing circuit of Figure Q4 (b) has current gain, $\beta=200$. Assume $V_{BE}=0.7V$.

- (i) Calculate the quiescent operating point. (5 marks)
- (ii) Sketch the load line with the proper labeling of saturation and cut off point. (4 marks)

 


Figure 4(b)

(c) Given the information provided in Figure Q4(c), assume determine

(i) β (3 marks)

(ii) V_{CC} (3 marks)

(iii) R_B (2 marks)

 


Figure Q4(c)

(d) Given the voltage-divider configuration network shown in Figure Q4(d). By using exact method, calculate

(i) I_C (4 marks)

(ii) V_{CE} (2 marks)

 


Figure Q4(d)

Question 5

- (a) Sketch the construction of D-MOSFET and E-MOSFET (n-channel). What is the difference between the operation of D-MOSFET and E-MOSFET? (5 marks)
- (b) For the JFET biasing network in Figure Q5(b),
- identify the type of network configuration. (2 marks)
 - determine I_{DQ} and V_{GSQ} . (5 marks)
 - determine V_{DS} . (2 marks)



 


Figure Q5(b)

 - (c) Find V_{GS} and V_{DS} for the E-MOSFET circuit in Figure Q5(c). Datasheet information is listed with the circuit. (7 marks)



- (d) Sketch the transfer characteristics for an n-channel enhancement type MOSFET from the drain characteristic given in Figure Q5 (d). (4 marks)

 

Question 6

- (a) Construct the block diagram of a basic DC voltage power supply with ac input voltage. Describe the function and sketch of output waveform of each module. (9 marks)
- (b) For the network of Figure Q6(b), calculate
- (i) the overall active, reactive and apparent power. (4 marks)
 - (ii) the power factor. (2 marks)
 - (iii) the total current, I_s . (3 marks)

 


Figure Q6(b)

- (c) The base bias circuit in Figure Q6(c) is subjected to a temperature variation from 0°C to 70°C . The β decrease by 50 percent at 0°C and increase by 75 percent at 70°C from its nominal value of 110 at 25°C . What are the % of changes in I_C over the temperature change from 0°C to 70°C ? (7 marks)

 


Figure Q6(c)

--THE END--

