

**INTI**  
**International College Penang**  
LAUREATE INTERNATIONAL UNIVERSITIES®

FINAL  
Examination Paper

(COVER PAGE)

Session : JANUARY 2015

Programmes : DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING  
(DEE)

Course : EEE1106 : ANALOGUE ELECTRONICS

Date of Examination : 10 March 2015

Time : 11.00 am – 1.00 pm Reading Time: Nil

Duration : 2 Hours

Special Instructions :

This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks.

**Students are not allowed to remove this question paper from the examination venue.**

Materials permitted : Non Programmable Scientific Calculator

Materials provided: Nil

Examiner(s) : Mr. Chan Tse Wei

Moderator : Dr. Khoo Bee Ee

*This paper consists of 8 printed pages, including the cover page.*

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)

**EEE1106 : ANALOGUE ELECTRONICS  
FINAL EXAMINATION : JANUARY 2015 SESSION**

**Instructions:** This paper consists of **SIX (6)** questions. Answer any **FOUR (4)** questions in the answer booklet provided. All questions carry equal marks. The marks allocated to each sub-question are shown in square brackets at the right-hand margin.

**Question 1**

- a. i. An amplifier has 5 dBm output power. Calculate its output power in Watts. [2]
- ii. The input and output resistances of a voltage amplifier are given as  $100\text{k}\Omega$  and  $200\Omega$  respectively. If the power gain of the amplifier is 40 dB, calculate its voltage gain in dB. [3]
- iii. The maximum voltage gain of an audio amplifier is found to be 50 dB. What is the voltage gain of the audio amplifier at its cutoff frequency? [2]
- iv. A voltage amplifier frequency response has a  $-40$  dB/dec roll off rate at the high frequency band. What does that mean? [2]
- b. Figure-Q1(b) shows a AC equivalent circuit model of a voltage amplifier at low frequency band. Determine the cutoff frequency of the amplifier. [6]

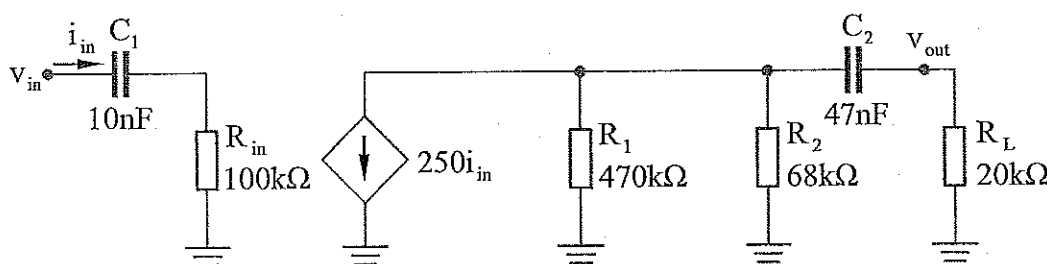


Figure-Q1(b)

- c. Determine the lower cutoff frequency (in Hz) of the amplifier circuit shown in Figure-Q1(c).  
Transistor  $Q_1$  has the following dynamic specifications:

Transconductance,  $g_m = 8 \text{ mS}$

Output resistance,  $r_d = \infty \Omega$

[10]

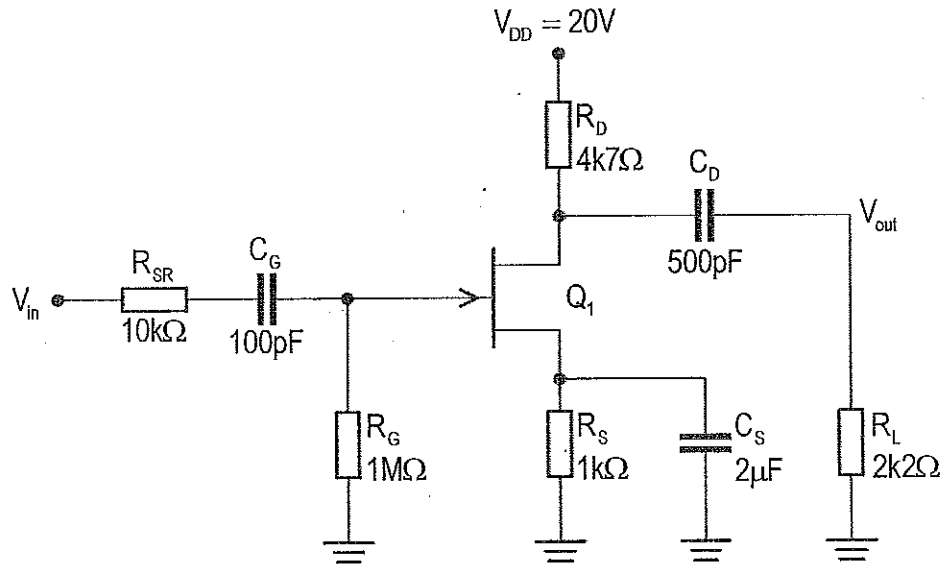


Figure-Q1(c)

## Question 2

- a. i. State the three main design features of a power amplifier. [3]
- ii. What is crossover distortion and which type of power amplifier exhibits crossover distortion in its output? [2]
- iii. State the two types of power amplifier which is biased for operation at more than  $180^\circ$  of the input cycle? [2]
- iv. State the function of power amplifiers and explain why it is always not 100% efficient. [3]
- b. A power amplifier circuit and its AC load line are shown in Figure-Q2(b)(i) and Figure-Q2(b)(ii) respectively. Also shown in Figure-Q2(b)(ii), are the amplifier's output voltage and its corresponding current swing. The wiring resistance and power dissipation of the transformer are negligible.
- i. From the given AC load line, calculate the transformer turn ratio,  $N:1$ . [3]
- ii. Calculate the power delivered to the  $8\Omega$  speaker. [2]
- iii. Calculate the DC power drawn from the supply. [2]

iv. Calculate the efficiency of the power amplifier. [2]

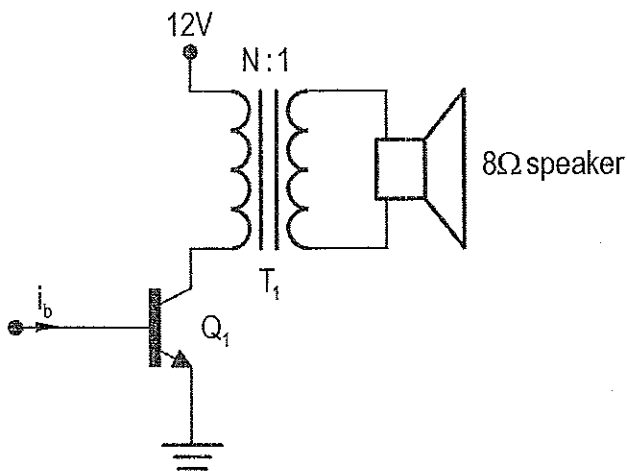


Figure-Q2(b)(i)

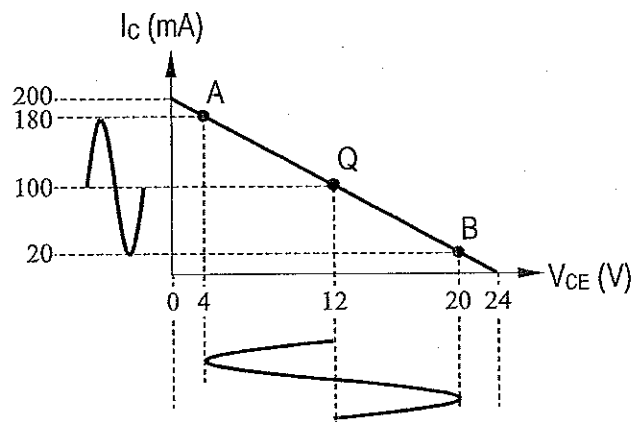


Figure-Q2(b)(ii)

c. Quantitatively show that the maximum theoretical efficiency of the power amplifier in Figure-Q2(b)(i) can be as high as 50%. [6]

### Question 3

a. i. Draw the circuit diagram of an active inverting integrator. [2]

ii. One application of the inverting integrator is to convert a square wave to a triangular wave. Describe the circuit operation that fulfills this implementation. [3]

iii. State two factors that limit the operation of the inverting integrator in fulfilling its application given in part (a)(ii). Explain your answer. [3]

b. i. State the name of the circuit implemented in Figure-Q3(b). [2]

ii. Determine the resistance ratio,  $R_1:R_2$  if the circuit's voltage transfer function is to be set at 100. [3]

iii. If the supply voltages for the op-amp is set at  $\pm 15V$  and its voltage transfer function is as given in part (b)(ii), determine the maximum allowable sinusoidal input voltage,  $V_{in}$  before the output voltage saturates. Assume ideal op-amp operation. [3]

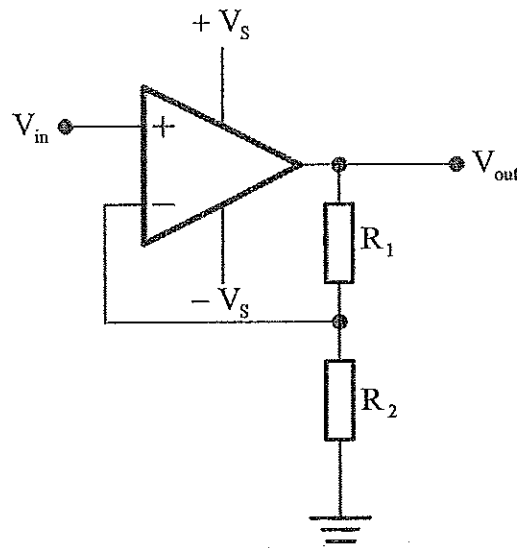


Figure-Q3(b)

- c. Base on the maximum allowable sinusoidal input voltage determined in part (b)(iii) and the voltage transfer function given in part (b)(ii), modify the circuit in Figure-Q3(b), assume ideal op-amp operation, so that it can be operated in single supply mode. Justify your modification(s).

[9]

#### Question 4

- a. The circuit shown in Figure-Q4(a) is to be utilized as a filter circuit.

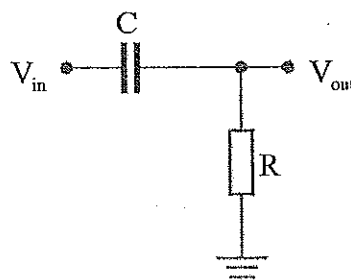


Figure-Q4(a)

- i. Identify the type of filter implemented. [2]
- ii. Identify the order of the filter. [2]
- iii. What is the expected roll-off rate of the filter? [2]
- iv. If the output terminal in Figure-Q4(a) is terminated by a resistor which is 5 times of  $R$ , how much (in percentage) will the cutoff frequency be increased or reduced? [4]

- b. Modify the circuit in Figure-Q4(a), by adding extra component, so that a resistive load terminating the output terminal will not affect the cutoff frequency set by the RC pair. Justify the modification made. [5]
- c. The circuit shown in Figure-Q4(c) is a multiple-feedback active filter circuit. The op-amp is assumed ideal.

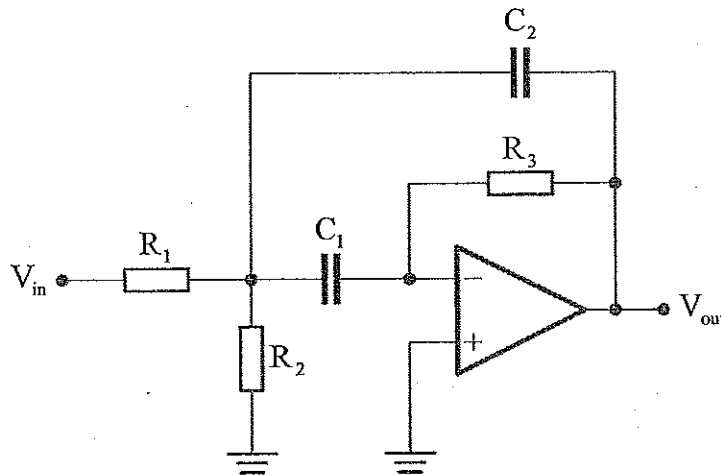


Figure-Q4(c)

- i. Derive the circuit's voltage transfer function. [5]
- ii. Hence, identify the type of filter implemented. [1]
- iii. If  $C_1 = C_2$ , show that the maximum magnitude of the voltage transfer function is,

$$\left| \frac{V_{out}}{V_{in}} \right|_{max} = \frac{R_3}{2R_1} \quad [4]$$

### Question 5

- a. i. Draw the block diagram of a RC feedback harmonic oscillator. [2]
- ii. State the Barkhausen criteria of oscillation used in RC feedback harmonic oscillator, clearly explain all the symbols used. [2]
- iii. State the condition where the oscillating waveform produced by a RC feedback harmonic oscillator shows signs of saturation, assuming that all components in the circuit are in working condition. [2]
- iv. State the condition where a RC feedback harmonic oscillator fails to produce a sinusoidal waveform, assuming that all components in the circuit are in working condition. [2]
- v. Name two examples of RC feedback harmonic oscillator. [2]
- b. i. Draw a schematic diagram of a relaxation oscillator that generates both square wave and triangular wave simultaneously. [2]
- ii. Briefly explain the operation of the oscillator given in part (b)(i). [3]
- c. Figure-Q5(c) shows FET-based oscillator circuit.

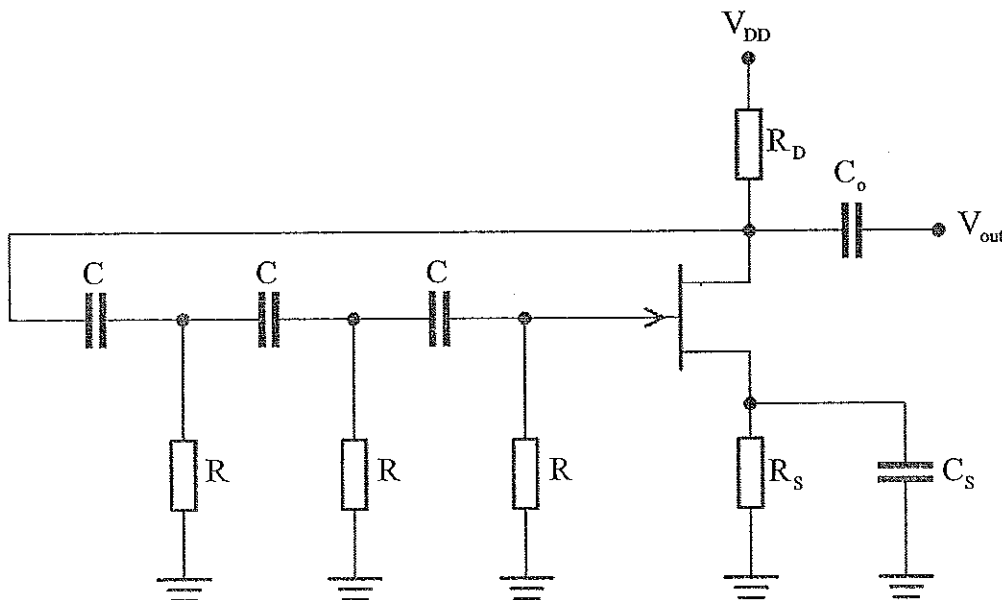


Figure-Q5(c)

- i. Draw the AC equivalent circuit model of the oscillator. The output dynamic drain-source resistance ( $r_d$ ) of the FET is not to be neglected. [2]
- ii. Hence, show that  $g_m(r_d // R_D) = 29$  when the circuit generate a sustainable sinusoidal output. Assume the feedback network draws negligible currents from the output. [8]

### Question 6

- a. i. Draw the schematic diagram of an inverting amplifier. [2]
- ii. Suggest relevant resistance values in the inverting amplifier given in part (a)(i) that fulfills the following design specifications: [3]
- Voltage gain,  $A_v = -8$
  - Input resistance,  $R_{in} = 20k\Omega$
- iii. If a 1V DC voltage is applied to the inverting amplifier designed in part (a)(ii) which is terminated by a  $1k\Omega$  load resistor, calculate the current flowing through to the  $1k\Omega$  load. [3]

- b. In addition to the design specifications listed in part (a)(ii), all the resistors used in the inverting amplifier circuit must be equal-valued and less than  $100k\Omega$  in order to minimize the impact of non-ideal characteristics of the op-amp used. Figure-Q6(b) shows a modified inverting amplifier that fulfills the new design requirements.

Show that the voltage gain of the amplifier is fulfilled. [7]

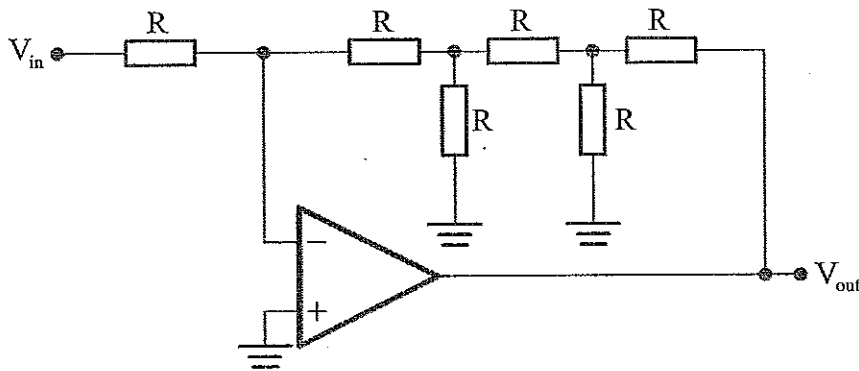


Figure-Q6(b)

- c. In a practical implementation of the circuit in Figure-Q6(b), a low graded op-amp is used to reduce the product cost. The op-amp has the following specifications:
- Input resistance,  $R_{in} = 100k\Omega$
  - Open-loop voltage gain,  $A_o = 1000$
  - Output resistance,  $R_{out} = 200\Omega$

Quantitatively investigate the effect of these specifications on the circuit voltage gain. [10]

– THE END –