



**FINAL  
ALTERNATIVE ASSESSMENT**

(COVER PAGE)

Session : January 2021

Programme : Diploma in Electrical & Electronic Engineering (DEEI)

Course : EEE2101: Introduction to Digital Electronics

Date of Examination : 9 March 2021 (Tuesday)

Time : 8.00am – 11.00am Reading Time : Nil

Duration : 3 Hours

**Special Instructions :**

This paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry equal marks.

---

Material permitted : Non-Programmable Scientific Calculator

Materials provided : Nil

Examiner(s) : Steven Khoo Boo Tap

Chief Moderator : Chan Tse Wei

*This paper consists of 8 printed pages, including the cover page*

INTI INTERNATIONAL COLLEGE PENANG

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING PROGRAMME (DEEI)  
 EEE2101: INTRODUCTION TO DIGITAL ELECTRONICS  
 FINAL ALTERNATIVE ASSESSMENT: JANUARY 2021 SESSION

Instructions: This paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry equal marks.

**Question 1**

(a) Present the following Boolean expressions according to the stated simplest form, using the specified method:

(i)  $F_1(W, X, Y, Z) = \sum m(3,7,12,14,15) + d(8,9,10)$

Simplest Form: POS.

Method: Karnaugh Map and/or Boolean Algebra.

(4 marks)

(ii)  $F_2(R, S, T, U) = \sum m(0,5,10,15) + d(3,6,9,12)$

Simplest Form: Any type of gate implementation deemed appropriate.

Method: Karnaugh Map and/or Boolean Algebra.

(4 marks)

(iii)  $F_3(K, L, M, N) = \prod M(0,2,4,6,8,10,13,15) \cdot \prod d(3,9)$

Simplest Form: Any type of gate implementation deemed appropriate.

Method: Karnaugh Map and/or Boolean Algebra.

(4 marks)

(b) Produce the simplest Boolean expression for F in Figure 1(b) and present the minimum expression using Boolean simplification method only. Suggest only one type of gate to represent the simplified expression and state the IC part number for the implementation. Show all workings clearly.

 


Figure 1(b)

(8 marks)

- (c) Solve the numbering system transformation of  $[3016.3016_{16} - 2021.2021_{16}]$  to its decimal equivalent with 5 decimal points accuracy. Show all workings clearly. (5 marks)

**Question 2**

- (a) A D flip-flop is connected as shown in Figure 2a(i). Sketch the output, Q with the given input, X waveform as shown in Figure 2a(ii). The output Q is initially HIGH. Assume that there is no propagation delay issue and the flip-flop has been enabled. Copy Figure 2a(ii) into your answer sheet.

 


Figure 2a(i)

 


Figure 2a(ii)

(5 marks)

- (b) A NOR SR latch is driven from a 2-bit binary counter with outputs designated  $B_1B_0$  ( $B_1$  is the MSB). Output  $B_1$  is ANDed with  $B_1 \oplus B_0$  and drives the R input of the SR latch.  $B_0$  is also ANDed with  $B_1 \oplus B_0$  and drives the S input.

- (i) Draw the logic circuit showing the inputs,  $B_1$  &  $B_0$  and output, Q of SR latch. (2.5 marks)
- (ii) Construct a truth table to record the output, Q of the SR latch as the counter steps through its 4 states beginning with  $B_1B_0 = 00$ . Assume the output is initially RESET. (2.5 marks)

- (c) A synchronous 3-bit up/down counter using positive edge-triggered JK flip-flop for MSB, D flip-flop for second bit and SR flip-flop for LSB. Assume  $J_2$  &  $K_2$  are the MSB input,  $D_1$  is the next flip-flop inputs and  $S_0$  &  $R_0$  are the LSB inputs. Assume all unused states as don't care.

Input S will be used as the up/down control. The counter will count from  $0 \Rightarrow 7 \Rightarrow 5 \Rightarrow 4 \Rightarrow 3 \Rightarrow 1 \Rightarrow 0$  when input,  $S = 0$  and  $0 \Rightarrow 1 \Rightarrow 3 \Rightarrow 4 \Rightarrow 5 \Rightarrow 7 \Rightarrow 0$  when input,  $S = 1$  as shown below in Figure 2(c). Flip-flop  $J_2K_2$  has output  $Q_2$ , flip-flop  $D_1$  has output  $Q_1$  and flip-flop  $S_0R_0$  has output  $Q_0$ .

Show all workings according to the procedures listed in part (c)(i), (c)(ii) and (c)(iii).

- (i) Prepare the transition table/next state table for the up/down counter. (4 marks)
- (ii) Produce the simplest Boolean expressions for  $J_2$ ,  $K_2$ ,  $D_1$ ,  $S_0$  and  $R_0$  inputs using Karnaugh map and/or Boolean algebra. (5 marks)
- (iii) Construct the logic circuit diagram for the simplified Boolean expressions obtained in part (c)(ii) using JK, D, SR flip-flops and other logic gates with proper labelling. (6 marks)

 


Figure 2(c)

**Question 3**

- (a) Solve the numbering system transformation of  $[10215.01_8 \times 16_8]$  to its hexadecimal equivalent with 2 hexadecimal points accuracy. Show all workings clearly. (5 marks)
- (b) Table 3(b) shows a portion of a quadruple 2-input NOR gates (SN54LS02) datasheet. Compute the following parameters from this datasheet, show all workings clearly:
  - (i) Power dissipation,  $P_{D(max)}$  on an SN54LS02 IC when the output condition is as shown in Figure 3(b). Assume that the  $V_{CC}$  used is maximum. (6 marks)

 


Figure 3(b)

- (ii) Fan-out, the number of gates from the same IC family that can be safely driven by an output under worst-case consideration. (3 marks)
- (iii) Noise Margin voltages,  $V_{NL}$  and  $V_{NH}$ . (3 marks)

Table 3(b)

GUARANTEED OPERATING RANGES						
Symbol	Parameter		Min	Typ	Max	Unit
$V_{CC}$	Supply Voltage	54 74	4.5 4.75	5.0 5.0	5.5 5.25	V
$T_A$	Operating Ambient Temperature Range	54 74	-55 0	25 25	125 70	$^{\circ}C$
$I_{OH}$	Output Current — High	54, 74			-0.4	mA
$I_{OL}$	Output Current — Low	54 74			4.0 8.0	mA

continue next page...

**DC CHARACTERISTICS OVER OPERATING TEMPERATURE RANGE** (unless otherwise specified)

Symbol	Parameter		Limits			Unit	Test Conditions
			Min	Typ	Max		
V <sub>IH</sub>	Input HIGH Voltage		2.0			V	Guaranteed Input HIGH Voltage for All Inputs
V <sub>IL</sub>	Input LOW Voltage	54			0.7	V	Guaranteed Input LOW Voltage for All Inputs
		74			0.8		
V <sub>IK</sub>	Input Clamp Diode Voltage			-0.65	-1.5	V	V <sub>CC</sub> = MIN, I <sub>IN</sub> = -18 mA
V <sub>OH</sub>	Output HIGH Voltage	54	2.5	3.5		V	V <sub>CC</sub> = MIN, I <sub>OH</sub> = MAX, V <sub>IN</sub> = V <sub>IH</sub> or V <sub>IL</sub> per Truth Table
		74	2.7	3.5		V	
V <sub>OL</sub>	Output LOW Voltage	54, 74		0.25	0.4	V	I <sub>OL</sub> = 4.0 mA
		74		0.35	0.5	V	I <sub>OL</sub> = 8.0 mA
I <sub>IH</sub>	Input HIGH Current				20	μA	V <sub>CC</sub> = MAX, V <sub>IN</sub> = 2.7 V
					0.1	mA	V <sub>CC</sub> = MAX, V <sub>IN</sub> = 7.0 V
I <sub>IL</sub>	Input LOW Current				-0.4	mA	V <sub>CC</sub> = MAX, V <sub>IN</sub> = 0.4 V
I <sub>OS</sub>	Short Circuit Current (Note 1)		-20		-100	mA	V <sub>CC</sub> = MAX
I <sub>CC</sub>	Power Supply Current Total, Output HIGH				3.2	mA	V <sub>CC</sub> = MAX
	Power Supply Current Total, Output LOW				5.4		

Note 1: Not more than one output should be shorted at a time, nor for more than 1 second.

**AC CHARACTERISTICS** (T<sub>A</sub> = 25°C)

Symbol	Parameter		Limits			Unit	Test Conditions
			Min	Typ	Max		
t <sub>PLH</sub>	Turn-Off Delay, Input to Output			10	15	ns	V <sub>CC</sub> = 5.0 V C <sub>L</sub> = 15 pF
t <sub>PHL</sub>	Turn-On Delay, Input to Output			10	15	ns	

(c) Table 3(c) shows the current ratings of TTL series logic gates. A 74S08 AND gate output is driving a few other TTL inputs as shown in Figure 3(c).

(i) Discover through calculation whether there is a loading problem.

(5 marks)

Table 3(c)

TTL Series	Output Drive		Input Loading	
	I <sub>OH</sub>	I <sub>OL</sub>	I <sub>IH</sub>	I <sub>IL</sub>
74	400μA	16mA	40μA	1.6mA
74S	1.0mA	20mA	50μA	2.0mA
74LS	400μA	8mA	20μA	400μA
74AS	2.0mA	20mA	200μA	2.0mA
74ALS	400μA	8mA	20μA	100μA
74F	1.0mA	20mA	20μA	600μA

- (ii) The 74S08 AND gate output needs to drive some 74S inputs in addition to the loads shown in Figure 3(c). Compute the additional number of 74S inputs that can be driven by the output of the 74S08 AND gate.

(3 marks)

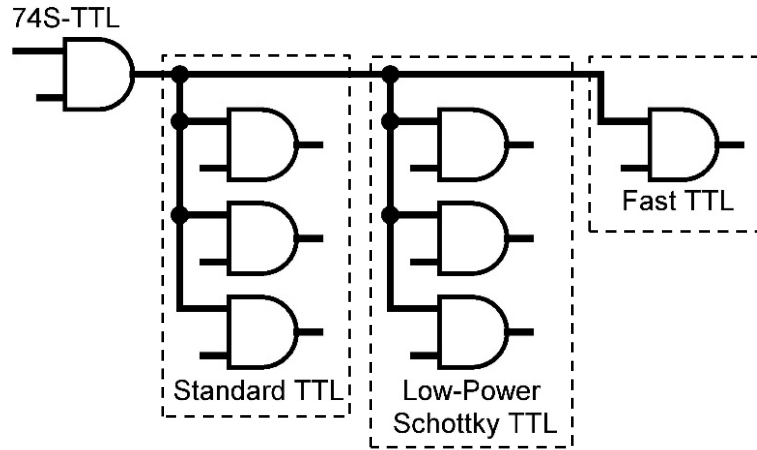


Figure 3(c)

**Question 4**

- (a) Compute the 2's complement number of  $-6.625_{10}$  in signed binary numbering system. Assuming the binary system is 4-bit system with 4 binary points. Show all workings clearly.

(5 marks)

- (b) A 14-bit DAC produces an output current in proportion to its digital input. For a digital input of  $00000001010000_2$ , an output current of 20mA is produced.

- (i) Compute the output current if the digital input is  $10010001111010_2$ .

(4 marks)

- (ii) Compute the maximum output current produced by this DAC.

(3 marks)

- (iii) Compute the digital input if a 2101mA output current is required.

(3 marks)

 


Figure 4(b)

- (c) Analog to Digital Converter (ADC) is an important element in signal processing for digital conversion of sensor signal. In the case of digitizing a vibration signal measured by an accelerometer (acceleration transducer) with the characteristics shown in Table 4(c).

Table 4(c)

<b>Sensitivity</b>	(±5.0%) 100 mV/g
<b>Measurement Range</b>	±50 g peak
<b>Frequency Range</b>	(±5%) 10 to 15000 Hz
<b>Sensing Element</b>	Quartz
<b>Weight</b>	100 gram

Assume the formula given is  $resolution = \frac{V_{range}}{2^n - 1}$ . Apply an appropriate ADC for this sensor application by computing the:

- (i) Number of bits. (7 marks)
- (ii) Resolution. (3 marks)

~THE END~

*EEE2101 (F)/ January 2021 Session/ formatted*